

- **Problem:** design a cyclic  $n$ -bit **counter**, i.e., a component whose output  $r$  steps through values

$$0, 1, \dots, 2^n - 1, 0, 1, \dots$$


but is otherwise uncontrolled (or “free running”).

- **Problem:** design a cyclic  $n$ -bit **counter**, i.e., a component whose output  $r$  steps through values

$$0, 1, \dots, 2^n - 1, 0, 1, \dots$$

but is otherwise uncontrolled (or “free running”).

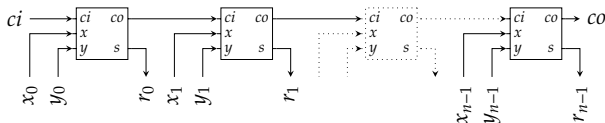- (Potential) **solution:** we already have an  $n$ -bit adder that can compute  $x + y$ , i.e.,




- **Problem:** design a cyclic  $n$ -bit **counter**, i.e., a component whose output  $r$  steps through values

$$0, 1, \dots, 2^n - 1, 0, 1, \dots$$

but is otherwise uncontrolled (or “free running”).

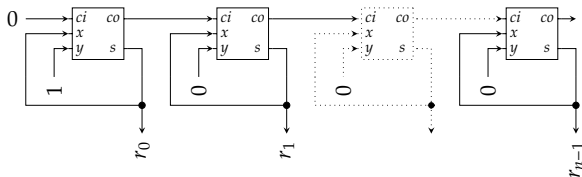- (Potential) **solution:** we already have an  $n$ -bit adder that can compute  $x + y$ , i.e.,




so we'll just have it compute  $r \leftarrow r + 1$  over and over again.

- **Problem:** design a cyclic  $n$ -bit **counter**, i.e., a component whose output  $r$  steps through values

$$0, 1, \dots, 2^n - 1, 0, 1, \dots$$

but is otherwise uncontrolled (or “free running”).

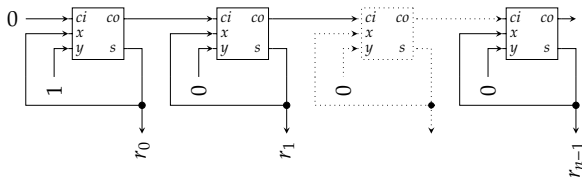- (Potential) **solution:** we already have an  $n$ -bit adder that can compute  $x + y$ , i.e.,



so we'll just have it compute  $r \leftarrow r + 1$  over and over again;

- (New) **problem:** this **won't work**, because, for example,
1. we can't initialise the value, and
  2. we don't let the output of each full-adder settle before it's used again as an input.

- ▶ (Actual) **problem**: combinatorial logic has some limitations, namely we can't
  - ▶ control *when* a design computes some output (it does so continuously), nor
  - ▶ *remember* the output when produced.
- ▶ (Actual) **solution**, and so **agenda**: **sequential logic** design, where, crucially,
  - ▶ the output is a function of the input plus any state (e.g., stemming from previous inputs),
  - ▶ computation is viewed as being discrete, i.e., step-by-step,


via coverage of

- |    |                                   |    |                                    |
|----|-----------------------------------|----|------------------------------------|
| 1. | synchronisation of components     | ~> | clocks                             |
| 2. | components that maintain state    | ~> | latches, flip-flops, and registers |
| 3. | mechanism for computational steps | ~> | structure plus strategy            |

## Part 1: clocks (1)

- **Concept:** a **clock** is a signal that oscillates (or alternates) between 1 and 0.

### Definition

 


where

- the clock signal is typically either
  1. an input which needs to be supplied externally, or
  2. produced internally by a **clock generator**.
- we use features of the clock to
  1. trigger events (e.g., steps in some sequence of computations), and/or
  2. synchronise components.
- the **clock frequency** is how many clock cycles happen per-second; it must be
  - fast enough to satisfy the design goals, yet
  - slow enough to cope with the critical path of a given step.

## Part 1: clocks (2)

- **Concept:** an  $n$ -phase clock is distributed as  $n$  separate signals along  $n$  separate wires.

### Definition

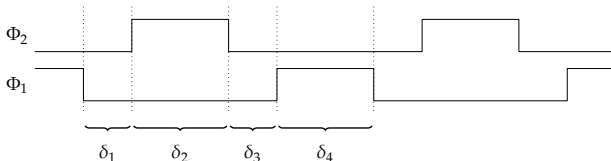

where for  $n = 2$ , for example,

- features in a 1-phase clock (e.g., cycle, levels and edges), generalise to  $\Phi_1$  and  $\Phi_2$ ,
- there is a guarantee that positive levels of  $\Phi_1$  and  $\Phi_2$  don't overlap, and
- the behaviour is parameterisable by altering  $\delta_i$ .

## Part 2: latches, flip-flops, and register (1)

### Concepts

#### Definition

A bistable component can exist in two stable states, i.e., 0 or 1: at a given point, it can

- ▶ retain some **current state**  $Q$  (which can also be read as an output), *and*
- ▶ be updated to some **next state**  $Q'$  (which is provided as an input)

under control of an **enable signal**  $en$ .

#### Definition

The behaviour of a bistable is described by an **excitation table**, and sometimes expressed using a **characteristic equation**: versus, e.g., a truth table, the idea is to capture the notion of time (cf. current and next).

#### Definition

A given bistable component controlled by an enable signal  $en$  can be

1. **level-triggered**, i.e., updated by a given level on  $en$ , or
2. **edge-triggered**, i.e., updated by a given edge on  $en$ .

The former type is termed a **latch**, whereas the latter type is termed a **flip-flop**.



## Part 2: latches, flip-flops, and register (2)

### Concepts

#### Definition

An “SR” latch/flip-flop component has two inputs  $S$  (or **set**) and  $R$  (or **reset**):

- ▶ when enabled, if
  - ▶  $S = 0$  and  $R = 0$ , the component retains  $Q$ ,
  - ▶  $S = 1$  and  $R = 0$ , the component updates to  $Q = 1$ ,
  - ▶  $S = 0$  and  $R = 1$ , the component updates to  $Q = 0$ ,
  - ▶  $S = 1$  and  $R = 1$ , the component is meta-stable
- but
- ▶ when not enabled, the component is in storage mode so retains  $Q$ .

The behaviour of such a component is specified by

$$Q' = S \vee (\neg R \wedge Q),$$

and/or

| $S$ | $R$ | Current |          | Next |           |
|-----|-----|---------|----------|------|-----------|
|     |     | $Q$     | $\neg Q$ | $Q'$ | $\neg Q'$ |
| 0   | 0   | 0       | 1        | 0    | 1         |
| 0   | 0   | 1       | 0        | 1    | 0         |
| 0   | 1   | ?       | ?        | 0    | 1         |
| 1   | 0   | ?       | ?        | 1    | 0         |
| 1   | 1   | ?       | ?        | ?    | ?         |

#### Definition

A “D” latch/flip-flop component has one input  $D$ :

- ▶ when enabled, if
  - ▶  $D = 1$ , the component updates to  $Q = 1$ ,
  - ▶  $D = 0$ , the component updates to  $Q = 0$ ,
- but
- ▶ when not enabled, the component is in storage mode so retains  $Q$ .

The behaviour of such a component is specified by

$$Q' = D,$$

and/or

| $D$ | Current |          | Next |           |
|-----|---------|----------|------|-----------|
|     | $Q$     | $\neg Q$ | $Q'$ | $\neg Q'$ |
| 0   | ?       | ?        | 0    | 1         |
| 1   | ?       | ?        | 1    | 0         |

## Part 2: latches, flip-flops, and register (3)

### Concepts

#### Definition

A “JK” latch/flip-flop component has two inputs  $J$  (or set) and  $K$  (or reset):

- ▶ when enabled, if
  - ▶  $J = 0$  and  $K = 0$ , the component retains  $Q$ ,
  - ▶  $J = 1$  and  $K = 0$ , the component updates to  $Q = 1$ ,
  - ▶  $J = 0$  and  $K = 1$ , the component updates to  $Q = 0$ ,
  - ▶  $J = 1$  and  $K = 1$ , the component toggles  $Q$ ,
- but
- ▶ when not enabled, the component is in storage mode so retains  $Q$ .

The behaviour of such a component is specified by

$$Q' = (J \wedge \neg Q) \vee (\neg K \wedge Q),$$

and/or

| $J$ | $K$ | Current |          | Next |           |
|-----|-----|---------|----------|------|-----------|
|     |     | $Q$     | $\neg Q$ | $Q'$ | $\neg Q'$ |
| 0   | 0   | 0       | 1        | 0    | 1         |
| 0   | 0   | 1       | 0        | 1    | 0         |
| 0   | 1   | ?       | ?        | 0    | 1         |
| 1   | 0   | ?       | ?        | 1    | 0         |
| 1   | 1   | 0       | 1        | 1    | 0         |
| 1   | 1   | 1       | 0        | 0    | 1         |

#### Definition

A “T” latch/flip-flop component has one input  $T$ :

- ▶ when enabled, if
  - ▶  $T = 0$ , the component retains  $Q$ ,
  - ▶  $T = 1$ , the component toggles  $Q$ ,
- but
- ▶ when not enabled, the component is in storage mode so retains  $Q$ .

The behaviour of such a component is specified by

$$Q' = (T \wedge \neg Q) \vee (\neg T \wedge Q) = T \oplus Q,$$

and/or


| $T$ | Current |          | Next |           |
|-----|---------|----------|------|-----------|
|     | $Q$     | $\neg Q$ | $Q'$ | $\neg Q'$ |
| 0   | 0       | 1        | 0    | 1         |
| 0   | 1       | 0        | 1    | 0         |
| 1   | 0       | 1        | 1    | 0         |
| 1   | 1       | 0        | 0    | 1         |

## Part 2: latches, flip-flops, and register (4)

Design(s)

- **Problem #1:** we need an initial design for, e.g., an SR latch.
- **Solution:** use two *cross-coupled* NOR gates.







### Circuit

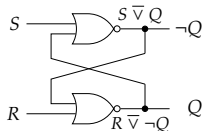

## Part 2: latches, flip-flops, and register (4)

Design(s)


- **Problem #1:** we need an initial design for, e.g., an SR latch.
- **Solution:** use two *cross-coupled* NOR gates.
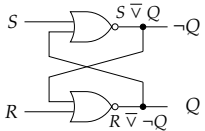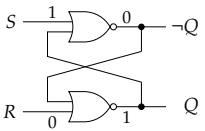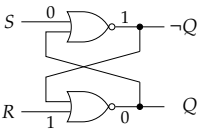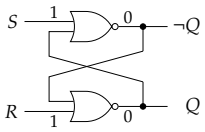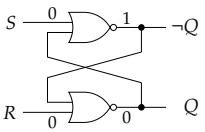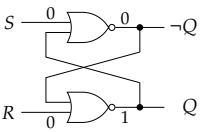
| Circuit   | Example ( $S = 1, R = 0, \checkmark$ )  | Example ( $S = 0, R = 1, \checkmark$ )   |
|---|---|--|
|  |  |  |
| Example ( $S = 1, R = 1, \times$ )  | Example ( $S = 0, R = 0, \checkmark$ )  | Example ( $S = 0, R = 0, \checkmark$ )   |
|  |  |  |
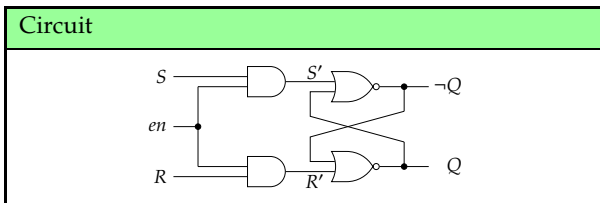
## Part 2: latches, flip-flops, and register (5)

Design(s)

- ▶ **Problem #2:** we'd like to control when updates occur.
- ▶ **Solution:** *gate*  $S$  and  $R$ , i.e.,



noting that

- ▶ the same internal latch is evident, now with inputs  $S'$  and  $R'$ ,
- ▶ the external latch is such that


$$\begin{aligned} en = 0 &\Rightarrow S' = S \wedge en = S \wedge 0 = 0 \\ &\Rightarrow R' = R \wedge en = R \wedge 0 = 0 \end{aligned}$$

$$\begin{aligned} en = 1 &\Rightarrow S' = S \wedge en = S \wedge 1 = S \\ &\Rightarrow R' = R \wedge en = R \wedge 1 = R \end{aligned}$$

## Part 2: latches, flip-flops, and register (6)

Design(s)

 - **Problem #3:** we'd like to avoid the issue of meta-stability.
- **Solution:** force  $R = \neg S$  so we get either  $S = 0$  and  $R = 1$ , or  $S = 1$  and  $R = 0$ .




## Part 2: latches, flip-flops, and register (7)

Design(s)


- **Problem #4:** we'd like an edge-triggered, rather than level-triggered design.
- **Solution #1:** "cheat" by approximation of an edge via a **pulse generator**.

### Circuit

The pulse generator component

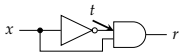

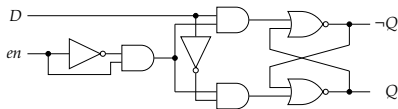is attached to the previous SR latch to give:




### Example

Imagine we set the delay of

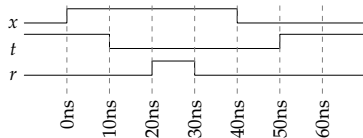1. a NOT gate to 10ns, and
2. an AND gate to 20ns

and then flip  $en = 0$  to  $en = 1$  and back again:




The result is a "pulse" matching the delay of a NOT gate that approximates an edge because it is so short.

## Part 2: latches, flip-flops, and register (8)

### Design(s)

- **Problem #4:** we'd like an edge-triggered, rather than level-triggered design.
- **Solution #2:** adopt a **primary-secondary** organisation of *two* latches, i.e.,

### Circuit

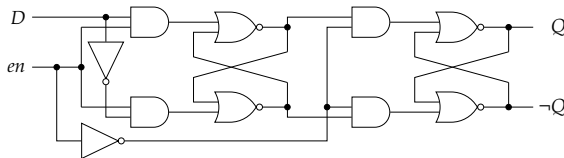

where the idea is to split a clock cycle into two half-cycles:

$en = 1 \Rightarrow$  **primary** latch is enabled

$en = 0 \Rightarrow$  **secondary** latch is enabled

meaning

1. *while*  $en = 1$ , i.e., positive level on  $en$ , primary latch stores input, and
2. *when*  $en = 0$ , i.e., negative edge on  $en$ , secondary latch stores output of primary latch, and hence we get edge-triggered behaviour.



## Part 2: latches, flip-flops, and register (9)


Abstraction, via symbols
 
### Definition

- ▶ A **D-type latch** is described symbolically as



- ▶ The associated behaviour is, for example,




such that updates are level-triggered by *en*.
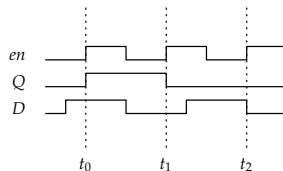
### Definition

- ▶ A **D-type flip-flop** is described symbolically as



- ▶ The associated behaviour is, for example,




such that updates are edge-triggered by *en*.

## Part 2: latches, flip-flops, and register (10)

Aggregation, via registers

- **Concept:** we typically combine latches (resp. flip-flops) into **registers**, i.e.,

### Circuit (latch version)

 

where

- there are  $n$  instances, so we can store an  $n$ -bit value: the  $i$ -th instance stores the  $i$ -th bit,
- access is conceptually straightforward:

read from register : use current value  $Q$

write to register : drive next value onto  $Q'$ , then trigger update via  $en$


- all instance share same  $en$ , so access to them is synchronised.

## Part 2: latches, flip-flops, and register (10)

Aggregation, via registers

- **Concept:** we typically combine latches (resp. flip-flops) into **registers**, i.e.,

### Circuit (flip-flop version)

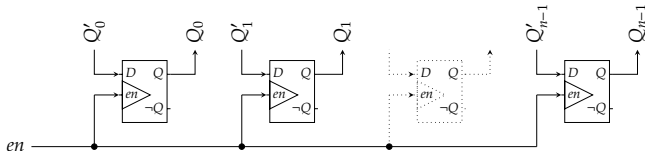

where

- there are  $n$  instances, so we can store an  $n$ -bit value: the  $i$ -th instance stores the  $i$ -th bit,
- access is conceptually straightforward:

read from register : use current value  $Q$


write to register : drive next value onto  $Q'$ , then trigger update via  $en$

- all instance share same  $en$ , so access to them is synchronised.

## Part 3: structure plus strategy (1)

Outcome: latch version, 2-phase clock


### Design (latch version)

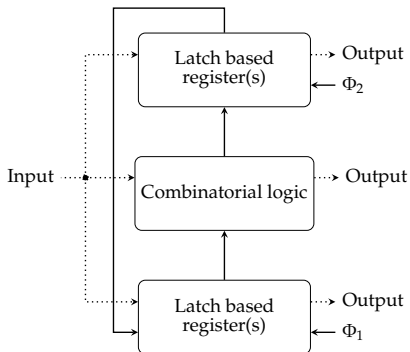

## Part 3: structure plus strategy (2)

Outcome: latch version, 2-phase clock


### Circuit (latch version)

 

## Part 3: structure plus strategy (3)

Outcome: latch version, 2-phase clock


### Example (latch version)

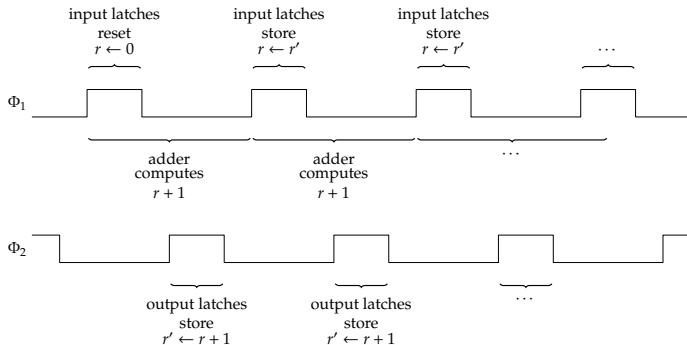

## Part 3: structure plus strategy (4)

Outcome: flip-flop version, 1-phase clock


### Design (flip-flop version)

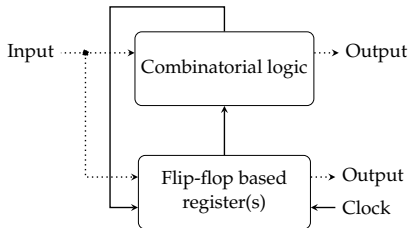

## Part 3: structure plus strategy (5)

Outcome: flip-flop version, 1-phase clock


### Circuit (flip-flop version)

 



Outcome: flip-flop version, 1-phase clock

### Example (flip-flop version)

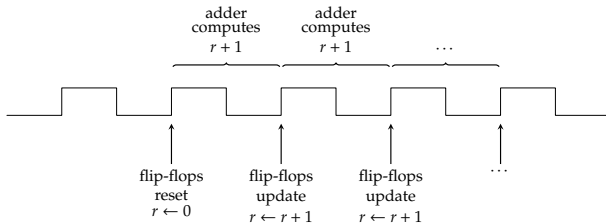

## ► Take away points:

1. Sequential logic design is typically hard(er) to understand (at first) than combinatorial logic design: invest some effort to address this now!
2. The main concept and challenge is *time*:
  - this goes beyond time in the sense of delay,
  - the goal is step-by-step, controlled (versus continuous, uncontrolled) computation,
  - we need to understand and manage, e.g., with parallelism and synchronisation.

### ► Take away points:

3. There is at least one higher-level design principle evident: we often see
  - a **data-path**, of computational and/or storage components, and
  - a **control-path**, that tells components in the data-path what to do and when to do it, although the counter control-path is (very) simple.
4. The next step is to formalise this, allowing solution of more complex problems, e.g., through more complex forms of control.

## Additional Reading

- ▶ *Wikipedia: Sequential logic*. URL: [https://en.wikipedia.org/wiki/Sequential\\_logic](https://en.wikipedia.org/wiki/Sequential_logic).
- ▶ D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009.
- ▶ W. Stallings. “Chapter 11: Digital logic”. In: *Computer Organisation and Architecture*. 9th ed. Prentice Hall, 2013.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.2.2: Clocks”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.3.4: Latches”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.3.4: Flip-flops”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.3.4: Registers”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.

# References

- [1] [Wikipedia: Sequential logic](https://en.wikipedia.org/wiki/Sequential_logic). URL: [https://en.wikipedia.org/wiki/Sequential\\_logic](https://en.wikipedia.org/wiki/Sequential_logic) (see p. 28).
- [2] D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009 (see p. 28).
- [3] W. Stallings. “Chapter 11: Digital logic”. In: *Computer Organisation and Architecture*. 9th ed. Prentice Hall, 2013 (see p. 28).
- [4] A.S. Tanenbaum and T. Austin. “Section 3.2.2: Clocks”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 28).
- [5] A.S. Tanenbaum and T. Austin. “Section 3.3.4: Flip-flops”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 28).
- [6] A.S. Tanenbaum and T. Austin. “Section 3.3.4: Latches”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 28).
- [7] A.S. Tanenbaum and T. Austin. “Section 3.3.4: Registers”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 28).