

- **Problem:** an  $n$ -bit register based on latches (resp. flip-flops) is limited in that
1. each latch (resp. flip-flop) in the register needs a relatively large number of transistors, which limits the viable capacity (i.e.,  $n$ ), and
  2. the register is not addressable, i.e.,
    - an **address** (or **index**) allows dynamic rather than static reference to some stored datum, so
    - by analogy, in a C program

## Listing

```

1  int A0, A1, A2, A3;
2
3  A0 = 0;
4  A1 = 0;
5  A2 = 0;
6  A3 = 0;
```


## Listing

```

1  int A[ 4 ];
2
3  A[ 0 ] = 0;
4  A[ 1 ] = 0;
5  A[ 2 ] = 0;
6  A[ 3 ] = 0;
```

we *have* the left-hand side, but we *want* the right-hand side.

 - **Solution:** a **memory** component, i.e.,



such that

- MEM has a capacity of  $n = 2^{n'}$  addressable words, and
- each such word is  $w$  bits (where  $n \gg w$ ).

### ► Agenda:

1. memory *cells*,
2. memory *devices*,

noting there are various ways to classify memories, e.g.,

1. volatility:
  - **volatile**, meaning the content is lost when the component is powered-off, or
  - **non-volatile**, meaning the content is retained even after the component is powered-off.
2. interface type:
  - **synchronous**, where a clock or pre-determined timing information synchronises steps, or
  - **asynchronous**, where a protocol synchronises steps.
3. access type:
  - random versus constrained (e.g., sequential) access to content,
  - **Random Access Memory (RAM)** which we can read from *and* write to, and
  - **Read Only Memory (ROM)** which, as suggested by the name, supports reads only.
4. ...


but we'll focus exclusively on a volatile, synchronous RAM.

## An Aside: some history



- ▶ The EDSAC used **delay line** memory, where the rough idea is:
  - ▶ Each “line” is a tube of mercury (or something else in which sound waves propagate fairly slowly).
  - ▶ Put a speaker at one end to store sound waves into the line, and a microphone at the other to read them out.
  - ▶ Values are stored in the sense the corresponding waves take time to propagate; when they get to one end they are either replaced or fed back into the other.
- ▶ This is **sequential access** (cf. **random access**): you need to *wait* for the data you want to appear!

## An Aside: some history

 

- ▶ The Whirlwind used **magnetic-core** memory, where the rough idea is:
  - ▶ The memory is a matrix of small magnetic rings, or “cores”, which can be magnetically polarised to store values.
  - ▶ Wires are threaded through the cores to control them, i.e., to store or read values.
  - ▶ The magnetic polarisation is retained, so core memory is non-volatile!
- ▶ You might still hear main memory termed **core memory** (cf. **core dump**) which is a throw-back to this technology.

[https://en.wikipedia.org/wiki/File:Project\\_Whirlwind\\_-\\_core\\_memory,\\_circa\\_1951\\_-\\_detail\\_1.JPG](https://en.wikipedia.org/wiki/File:Project_Whirlwind_-_core_memory,_circa_1951_-_detail_1.JPG)

## Part 1: memory cells (1)

### Comparison

#### Static RAM (SRAM) is

- ▶ manufacturable in lower densities (i.e., smaller capacity),
- ▶ more expensive to manufacture,
- ▶ fast(er) access time (resp. lower access latency),
- ▶ easy(er) to interface with,
- ▶ ideal for latency-optimised contexts, e.g., as cache memory.

### Comparison


#### Dynamic RAM (DRAM) is

- ▶ manufacturable in higher densities (i.e., larger capacity),
- ▶ less expensive to manufacture,
- ▶ slow(er) access time (resp. higher access latency),
- ▶ hard(er) to interface with,
- ▶ ideal for capacity-optimised contexts, e.g., as main memory.

## Part 1: memory cells (2)

An SRAM cell

### Circuit

 

#### ► Idea:

- internally, the cell is essentially two NOT gates,
- $bl$  and  $\neg bl$  are the **bit lines** (via which the state is accessed),
- $wl$  is the **word line** (which controls access to the state),
- a “6T SRAM cell” requires 6 transistors (cf.  $\sim 20$  or so for a D-type latch).

## An SRAM cell


- ▶ internally, the cell is essentially two NOT gates,
- ▶  $bl$  and  $\neg bl$  are the **bit lines** (via which the state is accessed),
- ▶  $wl$  is the **word line** (which controls access to the state),
- ▶ a “6T SRAM cell” requires 6 transistors (cf.  $\sim 20$  or so for a D-type latch).



## Part 1: memory cells (3)

### A DRAM cell

#### Circuit

 

- ▶ **Idea:**
  - ▶ internally, the cell is essentially one one transistor and one capacitor,
  - ▶ *bl* is the **bit line** (via which the state is accessed),
  - ▶ *wl* is the **word line** (which controls access to the state),
  - ▶ the capacitor
    1. discharges and charges (relatively) slowly,
    2. discharges when the cell is read, *and* also over time even if it's not read; this implies a need to **refresh** it.

## Part 2: memory cells $\leadsto$ memory devices (1)

► **Concept:** a **memory device** is constructed from (roughly) three components

1. a **memory array** (or matrix) of replicated cells with

- $r$  rows, and
- $c$  columns

meaning a  $(r \cdot c)$ -cell capacity,

2. a **row decoder** which given an address (de)activates associated cells in that row, and

3. a **column decoder** which given an address (de)selects associated cells in that column

plus additional logic to allow use (depending on cell type), e.g.,

1. **bit line conditioning** to, e.g., ensure the bit lines are strong enough to be effective, and
2. **sense amplifiers** to, e.g., ensure output from the array is usable.

## Part 2: memory cells $\leadsto$ memory devices (2)

An SRAM device: design

### ► (Typical, or exemplar) **design**: an **SRAM device**.

#### 1. interface:

- auxiliary pin(s) for power and so on,
- $D$ , a single 1-bit **data pin**,
- $A$ , a collection of  $n'$  **address pins** where  $A_i$  is the  $i$ -th such pin,
- a **Chip Select (CS)** pin, which enables the device,
- a **Output Enable (OE)** pin, which signals the device is being read from,
- a **Write Enable (WE)** pin, which signals the device is being written to.

## Part 2: memory cells $\leadsto$ memory devices (2)

An SRAM device: design

- (Typical, or exemplar) **design**: an **SRAM device**.

### 2. usage:

#### Algorithm (SRAM-READ)

Having performed the following steps

- drive the address onto  $A$ ,
- set  $WE = \text{false}$ ,  $OE = \text{true}$  and  $CS = \text{true}$ ,

1-bit of data is read and made available on  $D$ , then we set  $CS = \text{false}$ .

#### Algorithm (SRAM-WRITE)

Having performed the following steps


- drive the data onto  $D$ ,
- drive the address onto  $A$ ,
- set  $WE = \text{true}$ ,  $OE = \text{false}$  and  $CS = \text{true}$ ,

1-bit of data is written, then we set  $CS = \text{false}$ .

## Part 2: memory cells $\leadsto$ memory devices (3)


An SRAM device: implementation

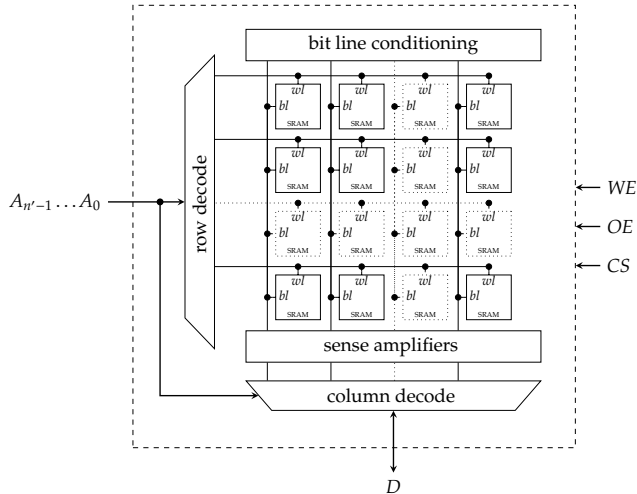Example (an  $n$ -cell SRAM device, for  $n = 2^{n'}$ )



## Part 2: memory cells $\leadsto$ memory devices (4)

### An SRAM device: implementation



**ASI**  
Austin Semiconductor, Inc.

**SRAM**  
**MT5C1001**  
**Limited Availability**

**1M x 1 SRAM**  
SRAM MEMORY ARRAY

**AVAILABLE AS MILITARY SPECIFICATIONS**

- MIL-STD-883C
- MIL-STD-883B

**FEATURES**

- High Speed: 20, 25, 35, and 45
- Battery Backup: 2V data retention
- Low power standby
- Single +5V (±10%) Power Supply
- Easy memory expansion with CE and OE options.
- All inputs and outputs are TTL-compatible
- Three-state output

**OPTIONS**

- Timing

**MARKING**

Timing	Marking
20ns access	-20
25ns access	-25
35ns access	-35
45ns access	-45
55ns access	-55
70ns access	-70*

**Packages**

Package	Marking	Part No.
Ceramic DIP (400mil)	C	No. 109
Ceramic LCC	EC	No. 207
Ceramic Flipchip	F	No. 303
Ceramic SOJ	DCJ	No. 501


**Operating Temperature Ranges**

Temperature Range	Marking
Industrial (-40°C to +85°C)	IT
Military (-55°C to +125°C)	MT


**2V data retention low power** L

\*Electrical characteristics identical to those provided for the 45ns access device.


**For more products and information please visit our web site at [www.austinsemiconductor.com](http://www.austinsemiconductor.com)**



28-Pin DIP (C)  
(400 MIL)



32-Pin LCC (EC)  
32-Pin SOJ (DC-J)



32-Pin Pin Pack (F)

**PIN ASSIGNMENT (Top View)**

**GENERAL DESCRIPTION**


The MT5C1001 employs low power, high-performance silicon-gate CMOS technology. Static design eliminates the need for external clocks or timing units while CMOS circuitry reduces power consumption and provides for greater reliability.

For flexibility in high-speed memory applications, ASI offers chip enable (CE) and output enable (OE) capability. These enhancements can place the outputs in High-Z for additional flexibility in system design. Writing to these devices is accomplished when write enable (WE) and CE inputs are both LOW. Reading is accomplished when WE remains HIGH while CE and OE go LOW. The devices offer a reduced power standby mode when disabled. This allows system designs to achieve low standby power requirements.

The "L" version provides an approximate 50 percent reduction in CMOS standby current ( $I_{CC1}$ ) over the standard version.

All devices operate from a single +5V power supply and all inputs and outputs are fully TTL-compatible.


MT5C1001  
Rev. 0.1 1/90



**ASI**  
Austin Semiconductor, Inc.

**SRAM**  
**MT5C1001**  
**Limited Availability**

**FUNCTIONAL BLOCK DIAGRAM**

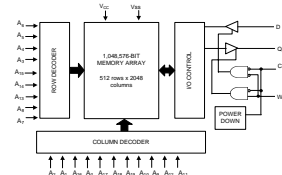

**TRUTH TABLE**

MODE	CE	WE	OUTPUT	POWER
STANDBY	H	A	HIGH-Z	STANDBY
READ	L	H	O	ACTIVE
WRITE	L	L	HIGH-Z	ACTIVE

**PIN ASSIGNMENTS**

PIN	ASSIGNMENT
A <sub>0</sub> -A <sub>15</sub>	Address Inputs
CE	Chip Enable
OE	Output Enable
D	Data Input
Q	Data Output
NO	No Connection
V <sub>CC</sub>	+5V Power Supply
V <sub>SS</sub>	Ground

MT5C1001  
Rev. 0.1 1/90

## Part 2: memory cells $\leadsto$ memory devices (5)

A DRAM device: interface

► (Typical, or exemplar) **design**: a **DRAM device**.

### 1. interface:

- auxiliary pin(s) for power and so on,
- $D$ , a single 1-bit **data pin**,
- $A$ , a collection of  $n'/2$  **address pins** where  $A_i$  is the  $i$ -th such pin,
- a **Chip Select (CS)** pin, which enables the device,
- a **Output Enable (OE)** pin, which signals the device is being read from,
- a **Write Enable (WE)** pin, which signals the device is being written to,
- a **Row Address Strobe (RAS)**, which controls the row buffer, and
- a **Column Address Strobe (CAS)**, which controls the column buffer.

## Part 2: memory cells $\leadsto$ memory devices (5)

A DRAM device: interface

- (Typical, or exemplar) **design**: a **DRAM device**.

### 2. usage:

#### Algorithm (DRAM-READ)

Having performed the following steps

- drive the row address onto  $A$ ,
- set  $RAS = \text{true}$  to latch row address,
- drive the column address onto  $A$ ,
- set  $CAS = \text{true}$  to latch column address,
- set  $WE = \text{false}$ ,  $OE = \text{true}$  and  $CS = \text{true}$ ,

1-bit of data is read and made available on  $D$ , then we set  $CS = RAS = CAS = \text{false}$ .

#### Algorithm (DRAM-WRITE)

Having performed the following steps

- drive the data onto  $D$ ,
- drive the row address onto  $A$ ,
- set  $RAS = \text{true}$  to latch row address,
- drive the column address onto  $A$ ,
- set  $CAS = \text{true}$  to latch column address,
- set  $WE = \text{false}$ ,  $OE = \text{true}$  and  $CS = \text{true}$ ,


1-bit of data is written, then we set  $CS = RAS = CAS = \text{false}$ .



## Part 2: memory cells $\leadsto$ memory devices (6)


### A DRAM device: implementation

 Example (a  $n$ -cell DRAM memory device, for  $n = 2^{n'}$ )



# Part 2: memory cells $\leadsto$ memory devices (7)

## A DRAM device: implementation


**AUSTIN SEMICONDUCTOR, INC.**

**MT4C1004J 883C**  
**4 MEG x 1 DRAM**

## DRAM

### 4 MEG x 1 DRAM

#### FAST PAGE MODE

**AVAILABLE AS MILITARY SPECIFICATIONS**

- SMD 3062 90622
- MIL-STD-883

**FEATURES**

- Industry standard x1 pinout, timing, functions and packages
- High performance, CMOS silicon gate process
- Single +5V 1.8V power supply
- Low power, 1.5mW standby; 300mW active, typical
- All inputs, outputs and clocks are fully TTL and CMOS compatible
- 1.624-cycle refresh distributed across 16ms
- Refresh modes: **EXCS-ONLY**, **CAS-BEFORE-EXCS** (CBBR), and **HIDDEN**
- **FAST PAGE MODE** access cycle
- CBBR with WE, a **HIGH** (HBBR) test mode capable via WCBRR

**OPTIONS**


- Timing
- 70ns access
- 80ns access
- 100ns access
- 120ns access

**MARKING**


	- 7	- 8	- 10	- 12
Ceramic DIP (883C)	CN	No. 881		
Ceramic DIP (883C)	C	No. 882		
Ceramic LCC	ECN	No. 883		
Ceramic SGP	ECT	No. 884		
Ceramic ZIP	CZ	No. 885		
Ceramic Gull Wing	ECG	No. 886		

**PIN ASSIGNMENT (Top View)**


**18-Pin DIP**



**20-Pin ZIP**



**20-Pin SOJ**  
**20-Pin LCC**  
**20-Pin Gull Wing**




\*Address not used for EXCS-ONLY, HBBR, CBBR

**GENERAL DESCRIPTION**

The MT4C1004 is a randomly accessed solid-state memory containing 4,096 1-bit cells organized in a 2K configuration. During **READ** or **WRITE** cycles, each bit is uniquely addressed through the 22 address bits which are entered 11 bits (A0-A10) at a time. **EXCS** is used to latch the first 11 bits and **CAS** the latter 11 bits. A **READ** or **WRITE** cycle is selected with the **WE** input. A high **HBBR** in **WE** initiates **READ** mode while a high **LOW** in **WE** initiates **WRITE** mode. During a **WRITE** cycle, data in (D) is latched by the

2-23

ASi Semiconductor, Inc. reserves the right to change product specifications without notice.


**AUSTIN SEMICONDUCTOR, INC.**


**MT4C1004J 883C**  
**4 MEG x 1 DRAM**

boundary. The **FAST PAGE MODE** cycle is always initiated with a row address strobed by the **EXCS** followed by a column address strobed by **CAS**. **CAS** may be toggled in by holding **EXCS** LOW and strobing in different column addresses, thus executing faster memory cycles. Raising **EXCS** HIGH terminates the **FAST PAGE MODE** operation, returning **EXCS** and **CAS** HIGH to maintain a memory cycle and decreases chip current to a reduced standby level. Also,

the chip is pre-conditioned for the next cycle during the **EXCS** HIGH time. Memory cell data is retained in the correct state by maintaining power and executing any **EXCS** cycle (**READ**, **WRITE**, **EXCS-ONLY**, **CAS-BEFORE-EXCS** or **HIDDEN-REFRESH**) so that all 1,024 combinations of **EXCS** addresses (A0-A9) are executed at least every 16ms, regardless of sequence. The **CAS-BEFORE-EXCS** cycle will invoke the refresh counter for automatic **EXCS** addressing.

### FUNCTIONAL BLOCK DIAGRAM

#### FAST PAGE MODE

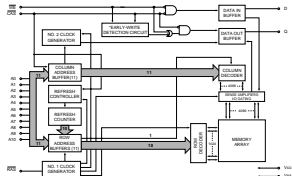

\*NOTE: **WE** LOW prior to **CAS** LOW. **EW** detection circuit output is a HIGH (**EARLY-WRITE**) **CAS** LOW prior to **WE** LOW. **EW** detection circuit output is a LOW (**LATE-WRITE**)

2-24

ASi Semiconductor, Inc. reserves the right to change product specifications without notice.

## Part 2: memory cells $\leadsto$ memory devices (9)

### ► Concept:

- *externally*, the configuration of a device is described as something like


$$\delta \times \omega \times \beta$$

(plus maybe some timing information) where

- $\delta$  relates to capacity, usually measured in (large multiples of) bits,
  - $\omega$  describes the width of words, measured in bits, and
  - $\beta$  is the number of internal **logical banks**.
- *internally*, this implies some organisational choices: for example,
1. for  $\omega > 1$ , we replicate the memory device internally to give  $\omega$  arrays (each copy relates to one bit of a  $\omega$ -bit word),
  2. for the arrays,  $r$  and  $c$  can be selected to match physical requirements (e.g., to get “square” or “thin” arrays), and
  3. for  $\beta > 1$ , each array is split into logical **banks**.


## Part 2: memory cells $\leadsto$ memory devices (10)
 
### Example (from a 1-bit to $w$ -bit SRAM device via replication)



## Part 2: memory cells $\leadsto$ memory devices (11)

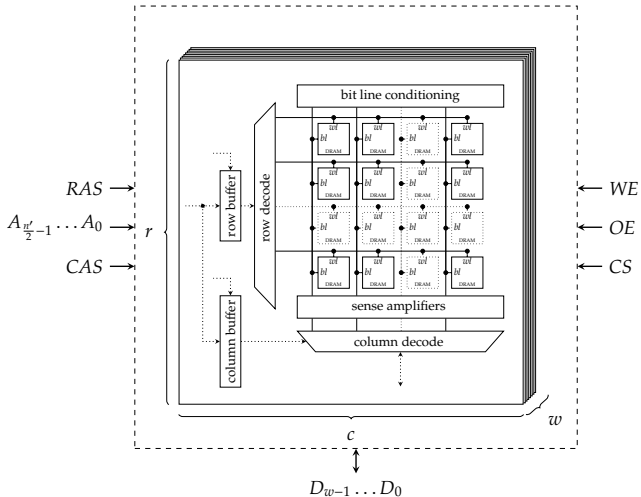Example (from a 1-bit to  $w$ -bit DRAM device via replication)



## ► Take away points:

1. The initial goal was an  $n$ -element memory of  $w$ -bit words; the final solution is motivated by divide-and-conquer, i.e.,
  - 1.1 one or more channels, each backed by
  - 1.2 one or more physical banks, each composed from
  - 1.3 one or more devices, each composed from
  - 1.4 one or more logical banks, of
  - 1.5 one or more arrays, of
  - 1.6 many cells
2. The major complication is a large range of increasingly detailed options:
  - lots of parameters mean lots of potential trade-offs (e.g., between size, speed and power consumption),
  - need to take care of detail: there are so many cells, any minor change can have major consequences!
3. Even so, there is just one key concept: we have some cells, and however they are organised we just need to identify and use the right cells given some address.

## Additional Reading

- ▶ *Wikipedia: Computer Memory*. URL: [https://en.wikipedia.org/wiki/Category:Computer\\_memory](https://en.wikipedia.org/wiki/Category:Computer_memory).
- ▶ D. Page. “Chapter 8: Memory and storage”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.3.5: Memory chips”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.3.6: RAMs and ROMs”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.
- ▶ W. Stallings. “Chapter 5: Internal memory”. In: *Computer Organisation and Architecture*. 9th ed. Prentice Hall, 2013.

# References

- [1] [Wikipedia: Computer Memory](https://en.wikipedia.org/wiki/Category:Computer_memory). URL: [https://en.wikipedia.org/wiki/Category:Computer\\_memory](https://en.wikipedia.org/wiki/Category:Computer_memory) (see p. 23).
- [2] D. Page. “Chapter 8: Memory and storage”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009 (see p. 23).
- [3] W. Stallings. “Chapter 5: Internal memory”. In: *Computer Organisation and Architecture*. 9th ed. Prentice Hall, 2013 (see p. 23).
- [4] A.S. Tanenbaum and T. Austin. “Section 3.3.5: Memory chips”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 23).
- [5] A.S. Tanenbaum and T. Austin. “Section 3.3.6: RAMs and ROMs”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 23).