

Computer Architecture

Daniel Page

Department of Computer Science,
University Of Bristol,
Merchant Venturers Building,
Woodland Road,
Bristol, BS8 1UB. UK.
(csdsp@bristol.ac.uk)

September 5, 2025

Keep in mind there are *two* PDFs available (of which this is the latter):

1. a PDF of examinable material used as lecture slides, and
2. a PDF of non-examinable, extra material:
 - ▶ the associated notes page may be pre-populated with extra, written explanation of material covered in lecture(s), plus
 - ▶ anything with a “grey’ed out” header/footer represents extra material which is useful and/or interesting but out of scope (and hence not covered).

Notes:

Notes:

Definition

In contrast to a conventional programming language which are (typically) used to describe software, a **Hardware Description Language (HDL)** is used to describe (or model) hardware (e.g., digital logic).

► (Selected) **examples**:

1. **Verilog**
2. **VHDL**
3. **MyHDL** \supset **Python**
4. **Chisel** \supset **Scala**
- ⋮

Notes:

Definition

In contrast to a conventional programming language which are (typically) used to describe software, a **Hardware Description Language (HDL)** is used to describe (or model) hardware (e.g., digital logic).

► (Selected) **examples**:

1. **Verilog**
2. **VHDL**
3. **MyHDL** \supset **Python**
4. **Chisel** \supset **Scala**
- ⋮

► **Agenda**: **Verilog**, or, more specifically,

1. foundational concepts,
2. low-level modelling,
3. high-level modelling, and
4. development concepts, e.g., testing and test stimuli.

► **Caveat!**

~ 2.5 hours \Rightarrow introductory coverage of *core* language features and workflow.

Notes:

Part 1: foundational concepts (1)

► **Question:** *why?*

► **Answer:** HDLs (and EDA tools more generally) help to

1. facilitate automation, e.g., with respect to

- simulation,
- verification, and
- translation

of what is a more clearly machine-readable design,


2. address the challenge of scale, e.g., with respect to design size and complexity.

Notes:

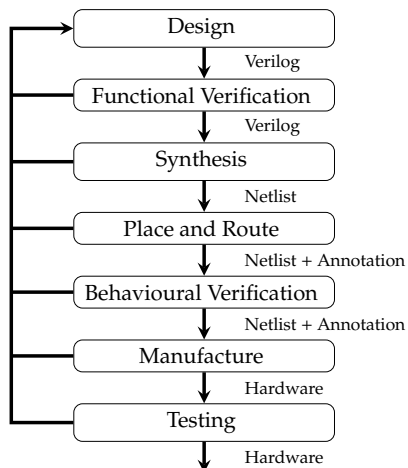Part 1: foundational concepts (2)

► **Question:** *how?*

► **Answer:** as part of a broader development workflow, such as



► You can think of

synthesis \approx compilation
place and route \approx linking

since

- the former translates from high- to low-level, in this case a HDL model to a gate-level netlist,
- the latter works out how to use the standard cell library (e.g., the type and location of gates).

► Verification steps rely on simulation of the model at different levels of detail.

Notes:

Part 1: foundational concepts (3)

► Analogy:

C	Verilog
<ul style="list-style-type: none">► A program is described using static function definitions.► Each function has an interface (i.e., what it does and how it can be used) and a body (i.e., how it does it).► The functions reference each other via calls; a function call implies an active, <i>transient</i> use.► Values are stored in variables, on which computation is performed by functions.	<ul style="list-style-type: none">► A model is described using static module definitions.► Each module has an interface (i.e., what it does and how it can be used) and a body (i.e., how it does it).► The modules reference each other via instantiations; a module instantiation implies an active, <i>permanent</i> use.► Values are carried by nets, on which computation is performed by modules.

but, beware:

- on one hand, the analogy is attractive if you have some C programming experience, *but*
- on the other hand, the analogy is unattractive (perhaps even *dangerous*) because it's *imperfect* in various ways.

Notes:

Part 1: foundational concepts (4)

► Example:

```
module fa( output wire co,
           output wire s,
           input wire ci,
           input wire x,
           input wire y );


  wire w0, w1, w2;

  xor t0( w0, x, y );
  and t1( w1, x, y );

  xor t2( s, w0, ci );
  and t3( w2, w0, ci );

  or t4( co, w1, w2 );

endmodule
```

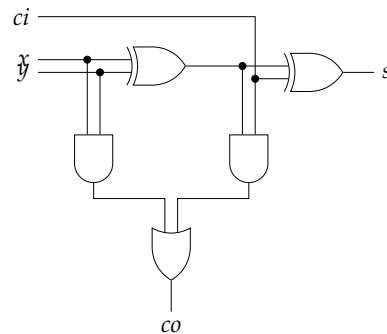

Notes:

Part 1: foundational concepts (5)

- **Example:** a model can be described in
1. a high-level, behaviour-oriented style, or
 2. a low-level, implementation-oriented style, or
 3. a *hybrid* of the two
- so, e.g.,

Option #1: switch-level Verilog

At the lowest-level, the model can be described using individual transistors. For example, the four transistor instances

```
pmos( t, VDD, b );  
pmos( a, t, c );  
nmos( a, VSS, c );  
nmos( a, VSS, b );
```

replicate the previous circuit for a MOSFET-based NOR gate, meaning they continuously drive the wire a with the the result of evaluating $\neg(b \vee c)$.

Notes:

Part 1: foundational concepts (5)

- **Example:** a model can be described in
1. a high-level, behaviour-oriented style, or
 2. a low-level, implementation-oriented style, or
 3. a *hybrid* of the two
- so, e.g.,

Option #2: gate-level Verilog

Forces the model to be described at a a low-level, using only primitive logic gates (e.g., AND, OR, NOT). For example, the gate instantiation

```
nor t( a, b, c );
```

continuously drives the wire a with the the result of evaluating $\neg(b \vee c)$.

Notes:

Part 1: foundational concepts (5)

- **Example:** a model can be described in
1. a high-level, behaviour-oriented style, or
 2. a low-level, implementation-oriented style, or
 3. a *hybrid* of the two
- so, e.g.,

Option #3: Register Transfer Level (RTL) Verilog

Uses a syntax similar to C, but focuses on describing the model in terms of the data-flow between components rather than high-level statements. For example, the continuous assignment

```
assign a = ~( b | c )
```

continuously drives the wire a with the the result of evaluating $\neg(b \vee c)$.

Notes:

Part 1: foundational concepts (5)

- **Example:** a model can be described in
1. a high-level, behaviour-oriented style, or
 2. a low-level, implementation-oriented style, or
 3. a *hybrid* of the two
- so, e.g.,

Option #4: behavioural-level Verilog

Allows a high-level, C-style description of the model using assignments, loops and conditional statements. For example, the procedural assignment

```
a = ~( b | c )
```

sets the register a equal to the result of evaluating $\neg(b \vee c)$.

Notes:

Part 2: low-level modelling (1)

Wires and values

► Concept: wires (resp. wire vectors)

► are a form of **net** used to *communicate* values,

► e.g.,

- wire `w` \Rightarrow an internal 1-bit wire `w`
- wire `[3 : 0] x` \Rightarrow an internal 4-bit wire vector `x`
- input wire `[3 : 0] y` \Rightarrow an input 4-bit wire vector `y`
- output wire `[3 : 0] z` \Rightarrow an output 4-bit wire vector `y`

Notes:

Part 2: low-level modelling (2)

Wires and values

► Concept: values

1. support the concept of 3-state logic, e.g.,

- `0` \Rightarrow 0 (i.e., logical **false**)
- `1` \Rightarrow 1 (i.e., logical **true**)
- `X` \Rightarrow unknown (i.e., neither 1 or 0)
- `Z` \Rightarrow high impedance (i.e., disconnected)

2. can be written in binary, decimal, or hexadecimal, e.g.,

- `2'b10` \Rightarrow a 2-bit binary literal, with value $10_{(2)}$, $2_{(10)}$, or $2_{(16)}$
- `8'd17` \Rightarrow a 8-bit decimal literal, with value $00010001_{(2)}$, $17_{(10)}$, or $11_{(16)}$
- `4'hF` \Rightarrow a 4-bit hexadecimal literal, with value $1111_{(2)}$, $15_{(10)}$, or $F_{(16)}$

3. can include 3-state values on a per-bit basis, e.g.,

- `1'bX` \Rightarrow a 1-bit binary literal; the bit is unknown
- `4'b10XZ` \Rightarrow a 4-bit binary literal; the bits are high impedance, unknown, 0, and 1

Notes:

Part 2: low-level modelling (3)

Wires and values

► Analogy:

C	Verilog
<ul style="list-style-type: none">► The definition $\text{char } u \rightsquigarrow 8 \text{ separate 1-bit elements}$ but u is typically used as 1 <i>single</i> 8-bit object.► The definition $\text{char } v[32] \rightsquigarrow 32 \text{ separate 8-bit elements}$ and v is typically used as 32 <i>separate</i> 8-bit elements.	<ul style="list-style-type: none">► The definition $\text{wire } x \rightsquigarrow 1 \text{ single 1-bit wire}$ and u is used as 1 <i>single</i> 1-bit object.► The definition $\text{wire } [3 : 0] y \rightsquigarrow 4 \text{ separate 1-bit wires}$ such that<ol style="list-style-type: none">1. y can be used as 1 <i>single</i> 4-bit object, <i>or</i>2. y can be used as 4 <i>separate</i> 1-bit wires.

but, beware:

- a wire (resp. wire vector) cannot retain state (e.g., doesn't behave like a C variable),
- we need to *drive* a value on it.


Notes:

Part 2: low-level modelling (4)

Wires and values

► Concept: subscript operator.

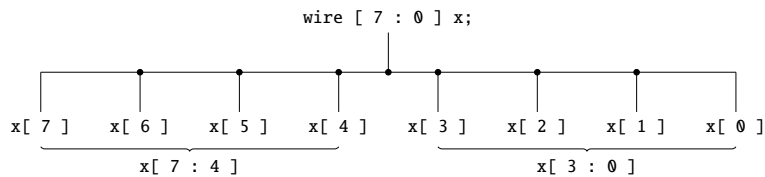- consider a case where $x = 8'b11110000$, and



- we have that

- $x[7]$, $x[6]$, $x[5]$ and $x[4]$ are all 1-bit wires with value 1'b1,
- $x[3]$, $x[2]$, $x[1]$ and $x[0]$, are all 1-bit wires with value 1'b0,
- $x[7 : 4]$ is a 4-bit wire vector with value 4'b1111, and
- $x[3 : 0]$ is a 4-bit wire vector with value 4'b0000.


Notes:

Part 2: low-level modelling (5)

Wires and values

► Concept: concatenate operator.

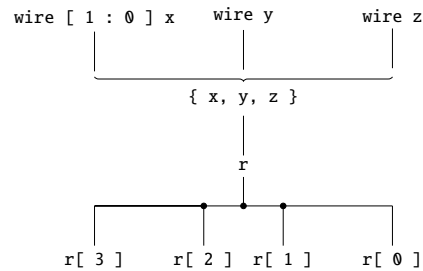- consider a case where $x = 2'b10$, $y = 1'b1$, and $z = 1'b0$, and



► we have that

- $\{ x, y, z \}$ is a 4-bit wire vector with value $4'b1010$,
- $r[3]$ is a 1-bit wire with value $1'b1$ (matching $x[1]$),
- $r[2]$ is a 1-bit wire with value $1'b0$ (matching $x[0]$),
- $r[1]$ is a 1-bit wire with value $1'b1$ (matching y), and
- $r[0]$ is a 1-bit wire with value $1'b0$ (matching z).


Notes:

Part 2: low-level modelling (6)

Wires and values

► Concept: replicate operator.

- consider a case where $x = 1'b1$, and

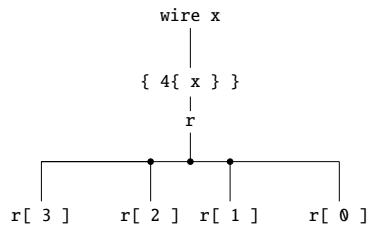

► we have that

- $\{ 4\{ x \} \}$ is a 4-bit wire vector with value $4'b1111$,
- $r[3]$ is a 1-bit wire with value $1'b1$,
- $r[2]$ is a 1-bit wire with value $1'b1$,
- $r[1]$ is a 1-bit wire with value $1'b1$, and
- $r[0]$ is a 1-bit wire with value $1'b1$.

Notes:

Part 2: low-level modelling (7)

Modules

► Concept: module **definition**

- are a passive (or static) *description* of a component,
- e.g.,

Listing (Verilog)	Listing (Verilog)
<pre>1 module mux2_1bit(output wire r, 2 input wire c, 3 input wire x, 4 input wire y); 5 6 ... 7 8 endmodule</pre>	<pre>1 module mux2_1bit(r, c, x, y); 2 3 output wire r; 4 input wire c; 5 input wire x; 6 input wire y; 7 8 ... 9 10 endmodule</pre>

noting the two forms are equivalent.


Notes:

Part 2: low-level modelling (8)

Modules

► Concept: module **instantiation**

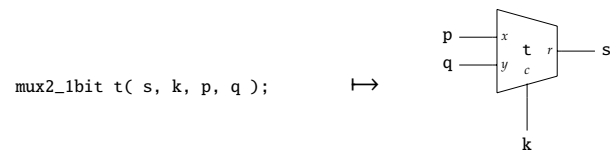- are an active (or dynamic) *use* of a component,
- e.g.,



where we've

- created an instance of the `mux2_1bit` module identified by `t`, and
- connected the internal ports `r`, `c`, `x` and `y` to the external wires `s`, `k`, `p` and `q`

Notes:

► **Analogy:**

C	Verilog
<ul style="list-style-type: none">► A caller function invokes (or calls) a callee function.► 1 <i>shared</i> copy of a callee function is used by <i>n</i> invocations.► Each invocation excutes in <i>sequence</i>, and <i>discontinuously</i>.	<ul style="list-style-type: none">► A instanciator module instantciates a instantiatee module.► <i>n separate</i> copies of a instantiatee module are produced by <i>n</i> instantciations.► Each instance operates in <i>parallel</i>, and <i>continuously</i>.

Notes:

► **Concept: gate-level module implementation**

- describes module behaviour via
 1. primitive (or built-in) modules, and/or
 2. other user-defined modules,
- e.g.,

buf t0(r, x);	↦	$r = x$
not t1(r, x);	↦	$r = \neg x$
nand t2(r, x, y);	↦	$r = x \overline{\wedge} y$
nor t3(r, x, y);	↦	$r = x \overline{\vee} y$
and t4(r, x, y);	↦	$r = x \wedge y$
or t5(r, x, y);	↦	$r = x \vee y$
xor t6(r, x, y);	↦	$r = x \oplus y$

noting that multi-input varients such as

xor t8(r, w, x, y);	↦	$r = w \oplus x \oplus y$
xor t9(r, w, x, y, z);	↦	$r = w \oplus x \oplus y \oplus z$

are automatically available.

Notes:

► **Concept: User-Defined Primitives (UDPs)**

- describe module behaviour via a truth table,
- doing so assumes it models a Boolean function of the form

$$f : \{0,1\}^n \rightarrow \{0,1\}$$

► e.g.,

Listing (Verilog)	Truth table																				
<pre>1 primitive mux2_1bit(output r, 2 input c, 3 input x, 4 input y); 5 6 table 7 0 0 ? : 0; 8 0 1 ? : 1; 9 1 ? 0 : 0; 10 1 ? 1 : 1; 11 endtable 12 endprimitive</pre>	<table><tr><th><i>c</i></th><th><i>x</i></th><th><i>y</i></th><th><i>r</i></th></tr><tr><td>0</td><td>0</td><td>?</td><td>0</td></tr><tr><td>0</td><td>1</td><td>?</td><td>1</td></tr><tr><td>1</td><td>?</td><td>0</td><td>0</td></tr><tr><td>1</td><td>?</td><td>1</td><td>1</td></tr></table>	<i>c</i>	<i>x</i>	<i>y</i>	<i>r</i>	0	0	?	0	0	1	?	1	1	?	0	0	1	?	1	1
<i>c</i>	<i>x</i>	<i>y</i>	<i>r</i>																		
0	0	?	0																		
0	1	?	1																		
1	?	0	0																		
1	?	1	1																		

which can then be used per a user-defined module.

Notes:

- In terms the UDP, there can be as many inputs as you like, there can be one output (which is *first* in the port list); both inputs and outputs *must* be 1-bit wires (i.e., wire vectors are not allowed).
- The ? symbol denotes don't care, meaning the first line can be read as “when c and x are both 0 and y is any value, set r to 0”.

► **Example:**

Listing (Verilog)	Circuit (full-adder)
<pre> 1 module fa(output wire co, 2 output wire s, 3 input wire ci, 4 input wire x, 5 input wire y); 6 7 wire w0, w1, w2; 8 9 xor t0(w0, x, y); 10 and t1(w1, x, y); 11 12 xor t2(s, w0, ci); 13 and t3(w2, w0, ci); 14 15 or t4(co, w1, w2); 16 17 endmodule </pre>	

Notes:

Part 2: low-level modelling (13)

Module implementation using gate-level Verilog

► Example:


Listing (Verilog)

```

1 module mux2_1bit( output wire r,
2                   input wire c,
3                   input wire x,
4                   input wire y );
5
6   wire w0, w1, w2;
7
8   not t0( w0, c );
9
10  and t1( w1, x, w0 );
11  and t2( w2, y, c );
12
13  or t3( r, w1, w2 );
14
15 endmodule

```

Circuit (2-input, 1-bit multiplexer)

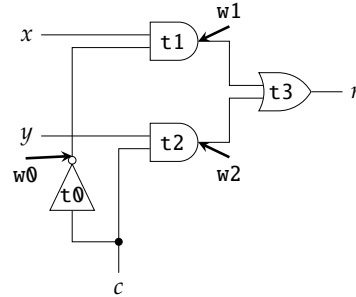

Notes:

Part 2: low-level modelling (14)

Module implementation using gate-level Verilog

► Example:


Listing (Verilog)

```

1 module mux2_4bit( output wire [ 3 : 0 ] r,
2                   input wire c,
3                   input wire [ 3 : 0 ] x,
4                   input wire [ 3 : 0 ] y );
5
6   mux2_1bit t0( r[ 0 ], c, x[ 0 ], y[ 0 ] );
7   mux2_1bit t1( r[ 1 ], c, x[ 1 ], y[ 1 ] );
8   mux2_1bit t2( r[ 2 ], c, x[ 2 ], y[ 2 ] );
9   mux2_1bit t3( r[ 3 ], c, x[ 3 ], y[ 3 ] );
10
11 endmodule

```

Circuit (2-input, 4-bit multiplexer)

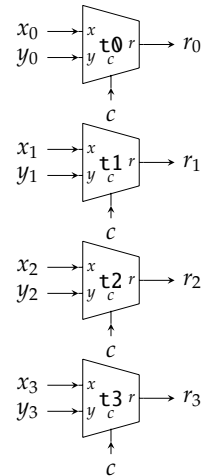

Notes:

► Example:


Listing (Verilog)

```

1 module mux4_1bit( output wire r,
2                   input wire c0,
3                   input wire c1,
4                   input wire w,
5                   input wire x,
6                   input wire y,
7                   input wire z );
8
9   wire w0, w1;
10
11  mux2_1bit t0( w0, c0, w, x );
12  mux2_1bit t1( w1, c0, y, z );
13  mux2_1bit t2( r, c1, w0, w1 );
14
15 endmodule

```

Circuit (4-input, 1-bit multiplexer)

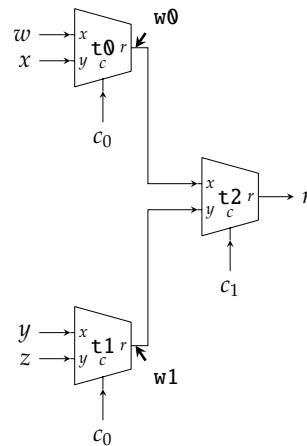


Notes:

Part 2: low-level modelling (16)
Module implementation using RTL-level Verilog

► Concept: Register Transfer Level (RTL) module implementation

- describes module behaviour via
 1. a set of **continuous assignments**, plus
 2. any additional gate-level description
- e.g.,

assign r = (x | y) & z; \mapsto or t0(w, x, y);
and t1(r, w, z); \mapsto

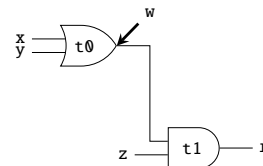

- the LHS *must* be a wire or wire vector, whereas
 - the RHS can contain many C-style operators
 - **arithmetic operators**, e.g., +, -, and *,
 - **logical operators**, e.g., <<, >>, ~, &, |, and ^,
 - **comparison operators**, e.g., ==, >, and <.
- involving wires or wire vectors as operands.

but, **beware:**

- it's tempting to think of this as analogous to a C assignment,
- this is dangerous, because the RTL version is *continuous*.

Notes:

► **Concept: reduction operator.**

- consider a case where `wire [3 : 0] x`, `wire [3 : 0] y`, and `wire c`,
- we have that

$$\text{^}x \mapsto ((x[3] \text{ ^} x[2]) \text{ ^} x[1]) \text{ ^} x[0]$$

so is analagous to reduce (or `foldr`) in Haskell.

Notes:

► **Concept: ternary operator.**

- consider a case where `wire [3 : 0] x`, `wire [3 : 0] y`, and `wire c`,
- we have that

$$c \text{ ? } y \text{ : } x \mapsto \begin{cases} x & \text{if } c = 0 \\ y & \text{if } c = 1 \end{cases}$$

so is analagous to a 2-input multiplexer.

Notes:

► Example:

Listing (Verilog)

```
1 module fa( output wire co,
2           output wire s,
3           input wire ci,
4           input wire x,
5           input wire y );
6
7   wire w0, w1, w2;
8
9   xor t0( w0, x, y );
10  and t1( w1, x, y );
11
12  xor t2( s, w0, ci );
13  and t3( w2, w0, ci );
14
15  or t4( co, w1, w2 );
16
17 endmodule
```

Listing (Verilog)

```
1 module fa( output wire co,
2           output wire s,
3           input wire ci,
4           input wire x,
5           input wire y );
6
7   wire [ 1 : 0 ] t;
8
9   assign t = ci + x + y;
10
11  assign s = t[ 0 ];
12  assign co = t[ 1 ];
13
14 endmodule
```

Notes:

► Example:

Listing (Verilog)

```
1 module fa( output wire co,
2           output wire s,
3           input wire ci,
4           input wire x,
5           input wire y );
6
7   wire w0, w1, w2;
8
9   xor t0( w0, x, y );
10  and t1( w1, x, y );
11
12  xor t2( s, w0, ci );
13  and t3( w2, w0, ci );
14
15  or t4( co, w1, w2 );
16
17 endmodule
```

Listing (Verilog)

```
1 module fa( output wire co,
2           output wire s,
3           input wire ci,
4           input wire x,
5           input wire y );
6
7   assign { co, s } = ci + x + y;
8
9 endmodule
```

Notes:

► Example:

Listing (Verilog)	Listing (Verilog)
<pre>1 module mux2_1bit(output wire r, 2 input wire c, 3 input wire x, 4 input wire y); 5 6 wire w0, w1, w2; 7 8 not t0(w0, c); 9 10 and t1(w1, x, w0); 11 and t2(w2, y, c); 12 13 or t3(r, w1, w2); 14 15 endmodule</pre>	<pre>1 module mux2_1bit(output wire r, 2 input wire c, 3 input wire x, 4 input wire y); 5 6 assign r = c ? y : x; 7 8 endmodule</pre>

Notes:

► Example:

Listing (Verilog)	Listing (Verilog)
<pre>1 module mux2_4bit(output wire [3 : 0] r, 2 input wire c, 3 input wire [3 : 0] x, 4 input wire [3 : 0] y); 5 6 mux2_1bit t0(r[0], c, x[0], y[0]); 7 mux2_1bit t1(r[1], c, x[1], y[1]); 8 mux2_1bit t2(r[2], c, x[2], y[2]); 9 mux2_1bit t3(r[3], c, x[3], y[3]); 10 11 endmodule</pre>	<pre>1 module mux2_4bit(output wire [3 : 0] r, 2 input wire c, 3 input wire [3 : 0] x, 4 input wire [3 : 0] y); 5 6 assign r = c ? y : x; 7 8 endmodule</pre>

Notes:

► Example:

Listing (Verilog)

```
1 module mux4_1bit( output wire r ,
2                   input wire c0,
3                   input wire c1,
4                   input wire w ,
5                   input wire x,
6                   input wire y,
7                   input wire z );
8
9   wire w0, w1, w2, w3, w4, w5;
10
11  not t0( w0, c0 );
12  not t1( w1, c1 );
13
14  and t2( w2, w0, w1, w );
15  and t3( w3, c0, w1, x );
16  and t4( w4, w0, c1, y );
17  and t5( w5, c0, c1, z );
18
19  or t6( r, w2, w3, w4, w5 );
20
21 endmodule
```

Listing (Verilog)

```
1 module mux4_1bit( output wire r ,
2                   input wire c0,
3                   input wire c1,
4                   input wire w ,
5                   input wire x,
6                   input wire y,
7                   input wire z );
8
9   assign r = c1 ? ( c0 ? z : y ) :
10              ( c0 ? x : w );
11
12 endmodule
```

Notes:

Part 3: high-level modelling (1)
Registers

► Concept: registers (resp. register vectors)


- are a form of **net** used to *store* values (i.e., retain state),
- e.g.,

- `reg w` \Rightarrow an internal 1-bit register `w`
- `reg [3 : 0] x` \Rightarrow an internal 4-bit register vector `x`

but, beware: registers *feel* analogous to C-style variables, but care is required re. use.

Notes:

► **Concept: module interfacing rules**

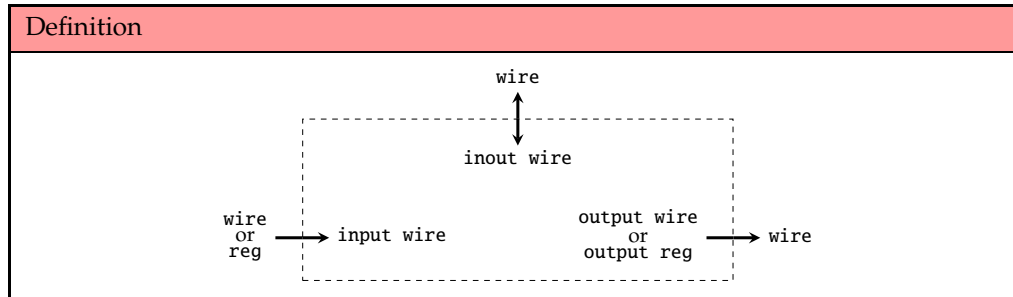

which are *somewhat* intuitive when read as

input port : $\begin{cases} \text{externally} & \text{can be a wire or reg} \\ \text{internally} & \text{must be a wire} \end{cases}$

output port : $\begin{cases} \text{internally} & \text{can be a wire or reg} \\ \text{externally} & \text{must be a wire} \end{cases}$

i.e., we must be pessimistic when crossing the module boundary.

Part 3: high-level modelling (3)
Module implementation using behavioural-level Verilog

► **Concept: behavioural-level module implementation**

- describes module behaviour via
 - (at least partly) using **processes**,
 - each process is formed from **blocks of statements**,
 - each process is “executed” in parallel with the others once **triggered**.
- e.g.,

Listing (Verilog)

```
1 initial begin: id
2   ...
3 end
```

Listing (Verilog)

```
1 always begin: id
2   ...
3 end
```

shows the two process types

- initial** \Rightarrow triggered only *once* (when the module is first powered-on)
- always** \Rightarrow triggered in a *loop* (as long as the module is powered-on)

noting the right-hand case is problematic as is ...

Notes:

- There is an extra port type in this diagram: an **inout** port models bi-directional (i.e., input *and* output) rather than uni-directional (i.e., input *or* output) communication.

Notes:

- There is an implicit dependence on time and therefore state: if statements are executed as steps in sequence, we need to “remember” values between steps.
- A statement (or block) *cannot* exist outside a process, and a process *cannot* exist outside a module; this would be analogous to writing an *if* statement outside any function in C for example.
- We *can* still mix styles, so it is okay to describe the behaviour of a module partly in RTL and partly as a behavioural process for example.
- Each behavioural process (or block) is composed *only* of behavioural statements: you can’t place other things in them, with examples including module instantiations (in an attempt to “call” a module like C function).

► **Concept: behavioural-level module implementation**

- describes module behaviour via
 - (at least partly) using **processes**,
 - each process is formed from **blocks of statements**,
 - each process is “executed” in parallel with the others once **triggered**.
- e.g.,

Listing (Verilog)	Listing (Verilog)	Listing (Verilog)
<pre>1 always @ (x) begin 2 ... 3 end</pre>	<pre>1 always @ (posedge x) begin 2 ... 3 end</pre>	<pre>1 always @ (negedge x) begin 2 ... 3 end</pre>

shows processes that are triggered via a **sensitivity list**:

- @ (x) ⇒ triggers when x changes
- @ (posedge x) ⇒ triggers when x changes from 0 to 1 (a positive edge)
- @ (negedge x) ⇒ triggers when x changes from 1 to 0 (a negative edge)

Notes:

- There is an implicit dependence on time and therefore state: if statements are executed as steps in sequence, we need to “remember” values between steps.
- A statement (or block) *cannot* exist outside a process, and a process *cannot* exist outside a module; this would be analogous to writing an `if` statement outside any function in C for example.
- We *can* still mix styles, so it is okay to describe the behaviour of a module partly in RTL and partly as a behavioural process for example.
- Each behavioural process (or block) is composed *only* of behavioural statements: you can’t place other things in them, with examples including module instantiations (in an attempt to “call” a module like C function).

► **Concept: procedural assignment, e.g.,**

Listing (Verilog)
<pre>1 module foo(input wire clk); 2 3 reg x, y; 4 5 always @ (posedge clk) begin 6 x = 1'b0; 7 y = 1'b1; 8 end 9 10 endmodule</pre>

which differ from a continuous assignment: they

1. must use a register as the LHS (versus a wire), and
2. the LHS is assigned to whatever the RHS evaluates to when the statement executes (versus whenever the RHS changes).

Notes:

- **Concept: procedural assignment**, e.g.,

Listing (Verilog)	
1	<code>module foo(input wire clk);</code>
2	
3	<code> reg x, y;</code>
4	
5	<code> always @ (posedge clk) begin</code>
6	<code> x = 1'b0;</code>
7	<code> y = 1'b1;</code>
8	<code> end</code>
9	
10	<code>endmodule</code>

which can introduce modelled **delay**:

- a **regular** delay, e.g.,

`#10 x = 0;`

means that, relative to the previous statement, this one will execute 10 time units later, whereas

- an **intra-assignment** delay, e.g.,

`x = #10 0;`

means that the RHS is evaluated straight away, but only assigned to the LHS after 10 time units.

Notes:

- **Concept: procedural assignment**, e.g.,

Listing (Verilog)	
1	<code>module foo(input wire clk);</code>
2	
3	<code> reg x, y;</code>
4	
5	<code> always @ (posedge clk) begin</code>
6	<code> x = 1'b0;</code>
7	<code> y = 1'b1;</code>
8	<code> end</code>
9	
10	<code>endmodule</code>

which come in **blocking** or **non-blocking** variants:

- if we write

`x = 0; y = 1;`

then the assignment to y is blocked until the assignment to x is executed, whereas

- if we write

`x <= 0; y <= 1;`

then the assignments to x and y are executed in parallel.

Notes:

Module implementation using behavioural-level Verilog

- **Concept:** conditional statements, e.g.,

Listing (Verilog)	Listing (Verilog)
<pre> 1 module bar(input wire clk); 2 3 reg x, y; 4 5 always @ (posedge clk) begin 6 if(x == 1'b0) begin 7 y = 1'b1; 8 end else begin 9 y = 1'b0; 10 end 11 end 12 13 endmodule </pre>	<pre> 1 module baz(input wire clk); 2 3 reg x, y; 4 5 always @ (posedge clk) begin 6 case(x) 7 1'b0 : y = 1'b1; 8 1'b1 : y = 1'b0; 9 default : y = 1'b0; 10 endcase 11 end 12 13 endmodule </pre>

noting that

- ▶ it starts to be attractive to leave out the begin and end keywords for single line blocks; this is equivalent to the same rule with “curly braces” in C,
- ▶ we need to take care with unknown or high impedance values; if x doesn't equal 0 or 1 you may get unexpected behaviour.

Notes:

Module implementation using behavioural-level Verilog

- Example:

Listing (Verilog)

```

1 module dff( input wire en,
2
3         input wire D,
4         output wire Q );
5
6     wire w0, w1, w2, w3, w4, w5, w6, w7;
7
8     not t0( w0, en );
9     and t1( w1, w0, en );
10
11    buf t2( w2, D );
12    not t3( w3, D );
13
14    and t4( w4, w2, w1 );
15    and t5( w5, w3, w1 );
16
17    nor t6( w6, w4, w7 );
18    nor t7( w7, w5, w6 );
19
20    buf t8( Q, w7 );
21
22 endmodule
                
```

Circuit

Notes:

► Example:

Listing (Verilog)	Circuit
<pre>1 module dff(input wire en, 2 3 input wire D, 4 output wire Q); 5 6 reg t; 7 8 assign Q = t; 9 10 always @ (posedge en) begin 11 t = D; 12 end 13 14 endmodule</pre>	


Notes:

► Example:

Algorithm	Listing (Verilog)
	<pre>1 module fsm(input wire clk, 2 3 output wire r, 4 input wire X); 5 6 reg Q; 7 8 assign r = (Q == 1'b0); 9 10 initial begin 11 Q = 1'b0; 12 end 13 14 always @ (posedge clk) begin 15 case({ Q, X }) 16 { 1'b0, 1'b0 } : Q = 1'b1; 17 { 1'b0, 1'b1 } : Q = 1'b0; 18 { 1'b1, 1'b0 } : Q = 1'b0; 19 { 1'b1, 1'b1 } : Q = 1'b1; 20 endcase 21 end 22 23 endmodule</pre>


Notes:

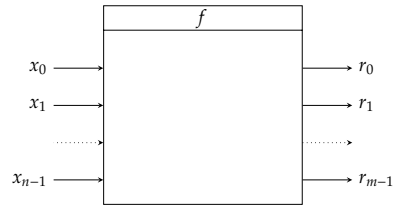► **Concept:** test stimulus (or test harness).



Notes:

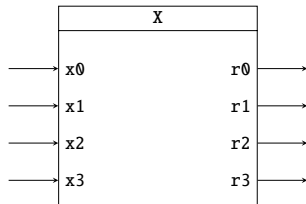► **Concept:** test stimulus (or test harness).




Notes:

 Part 4: development concepts (1)

Testing

► **Concept:** test stimulus (or test harness).




Notes:

 Part 4: development concepts (1)


Testing

► **Concept:** test stimulus (or test harness).



Notes:

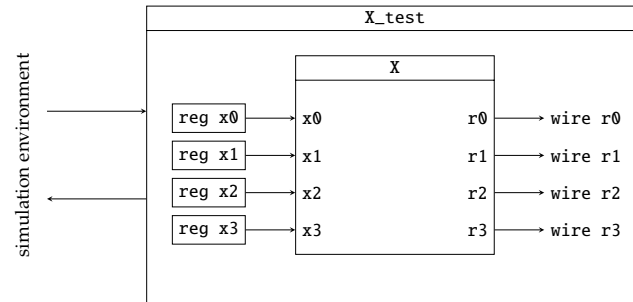► **Concept: test stimulus (or test harness)**



noting that **X_test**

- is termed a (or the) **top-level module** in the sense it has no inputs or outputs,
- can interact with the simulation environment via **system tasks** and **system functions**, e.g.,
 - \$random ⇒ generates random value(s)
 - \$display ⇒ displays value(s) synchronously
 - \$monitor ⇒ displays value(s) asynchronously
 - \$stop ⇒ halt current simulation
 - \$finish ⇒ terminate current simulation
- will apply some form of **test strategy** to the instance of **X**.

Notes:

► **Example:**

Listing (Verilog)

```
1 module fa_test();
2
3   wire t_co,      t_s;
4   reg  t_ci; t_x, t_y;
5
6   fa t( .co( t_co ), .s( t_s ), .ci( t_ci ), .x( t_x ), .y( t_y ) );
7
8   initial begin
9     #10 t_ci = 1'b0; t_x = 1'b0; t_y = 1'b0;
10    #10 $display( "co=%b s=%b ci=%b x=%b y=%b", t_co, t_s, t_ci, t_x, t_y );
11    #10 t_ci = 1'b0; t_x = 1'b0; t_y = 1'b1;
12    #10 $display( "co=%b s=%b ci=%b x=%b y=%b", t_co, t_s, t_ci, t_x, t_y );
13    #10 t_ci = 1'b0; t_x = 1'b1; t_y = 1'b0;
14    #10 $display( "co=%b s=%b ci=%b x=%b y=%b", t_co, t_s, t_ci, t_x, t_y );
15    #10 t_ci = 1'b0; t_x = 1'b1; t_y = 1'b1;
16    #10 $display( "co=%b s=%b ci=%b x=%b y=%b", t_co, t_s, t_ci, t_x, t_y );
17
18    #10 $finish;
19  end
20
21 endmodule
```

Notes:

► Example:

Listing (Verilog)

```
1 module fa_test();
2
3   wire t_co,      t_s;
4   reg  t_ci; t_x, t_y;
5
6   fa t( .co( t_co ), .s( t_s ), .ci( t_ci ), .x( t_x ), .y( t_y ) );
7
8   initial begin
9       $monitor( "co=%b s=%b ci=%b x=%b y=%b", t_co, t_s, t_ci, t_x, t_y );
10
11       $monitoron;
12
13       #10 t_ci = 1'b0; t_x = 1'b0; t_y = 1'b0;
14       #10 t_ci = 1'b0; t_x = 1'b0; t_y = 1'b1;
15       #10 t_ci = 1'b0; t_x = 1'b1; t_y = 1'b0;
16       #10 t_ci = 1'b0; t_x = 1'b1; t_y = 1'b1;
17
18       #10 $monitoroff;
19       $finish;
20   end
21
22 endmodule
```

Notes:

Part 4: development concepts (4)
“Quality-of-life” features

► **Concept:** a “better” model \leadsto greater **generalisation, maintainability**, etc.

1. We can use a **pre-processor** to
 - define symbolic names for literals, e.g.,

```
`define TRUE 1
```

then

- use those symbolic names e.g.,

```
assign r = x ^ `TRUE;
```

2. We can use **named ports** to avoid misconnections, e.g.,
fa t(.co(a), .s(b), .ci(c), .x(d), .y(e));

is the same as

```
fa t( .co(a), .s(b), .ci(c), .y(e), .x(d) );
```

3. We can **parametrise** modules:
 - their interface and behaviour is specified by a *single* fragment of source code,
 - each instance can be altered to suit the context it is used in.
4. We can **generate** “regular” fragments of source code (cf. meta-programming, versus “copy and paste”).

Notes:

► Example:

```
Listing (Verilog)
1 `define N 8
2
3 module mux2_nbit( output wire [ `N - 1 : 0 ] r,
4                  input wire c,
5                  input wire [ `N - 1 : 0 ] x,
6                  input wire [ `N - 1 : 0 ] y );
7
8     assign r = c ? y : x;
9
10 endmodule
```

Notes:

► Example:

```
Listing (Verilog)
1 module mux2_1bit( output wire r,
2                  input wire c,
3                  input wire x,
4                  input wire y );
5
6 `ifdef GATES
7     wire w0, w1, w2;
8
9     not t0( w0, c );
10
11     and t1( w1, x, w0 );
12     and t2( w2, y, c );
13
14     or t3( r, w1, w2 );
15 `else
16     assign r = c ? y : x;
17 `endif
18
19 endmodule
```

Notes:

► Example:

Listing (Verilog)	Listing (Verilog)
<pre>1 module mux2_nbit(r, c, x, y); 2 3 parameter N = 1; 4 5 output wire [N - 1 : 0] r; 6 input wire c; 7 input wire [N - 1 : 0] x; 8 input wire [N - 1 : 0] y; 9 10 assign r = c ? y : x; 11 12 endmodule</pre>	<pre>1 module mux2_4bit(output wire [3 : 0] r, 2 input wire c, 3 input wire [3 : 0] x, 4 input wire [3 : 0] y); 5 6 mux2_nbit t(r, c, x, y); 7 8 defparam t.N = 4; 9 10 endmodule 11 12 module mux2_8bit(output wire [7 : 0] r, 13 input wire c, 14 input wire [7 : 0] x, 15 input wire [7 : 0] y); 16 17 mux2_nbit t(r, c, x, y); 18 19 defparam t.N = 8; 20 21 endmodule</pre>

Notes:

► Example:

Listing (Verilog)	Listing (Verilog)
<pre>1 module mux2_4bit(output wire [3 : 0] r, 2 input wire c, 3 input wire [3 : 0] x, 4 input wire [3 : 0] y); 5 6 mux2_1bit t0(r[0], c, x[0], y[0]); 7 mux2_1bit t1(r[1], c, x[1], y[1]); 8 mux2_1bit t2(r[2], c, x[2], y[2]); 9 mux2_1bit t3(r[3], c, x[3], y[3]); 10 11 endmodule</pre>	<pre>1 module mux2_4bit(output wire [3 : 0] r, 2 input wire c, 3 input wire [3 : 0] x, 4 input wire [3 : 0] y); 5 6 genvar i; 7 8 generate 9 for(i = 0; i < 4; i = i + 1) begin:id 10 mux2_1bit t(r[i], c, x[i], y[i]); 11 end 12 endgenerate 13 endmodule</pre>

Notes:

Conclusions

- Take away points:

1. In essence, a HDL model is just machine-readable short-hand for a design you could develop and reason about on paper.
2. It's important to remember that, despite appearances,

HDL modelling \neq software development,

i.e., you *still* have to understand the fundamentals and “think in hardware”.


3. Even within this unit, HDLs offer various useful properties, e.g.,
 - ▶ adopt a more accurate experimental approach to design,
 - ▶ deal with designs of a larger scale,
 - ▶ interface with other concepts (e.g., verification),
 - ▶ ...

so some up-front, invested effort *could* pay off ...

Notes:

Conclusions

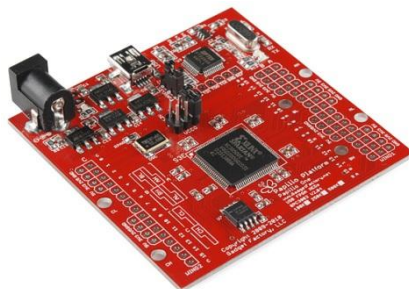- **Example:** Field Programmable Gate Arrays (FPGAs).



- ▶ basic idea is that the hardware fabric is reconfigurable, so, in a sense,

hardware (e.g., ASIC) hybrid (e.g., FPGA) software (e.g., micro-processor)


- ▶ and therefore offers a trade-off:

efficiency \simeq hardware
flexibility \simeq software


Notes:

Conclusions

 ► Example: Field Programmable Gate Arrays (FPGAs).



 - basic idea is that the hardware fabric is reconfigurable, so, in a sense,




- and therefore offers a trade-off:

efficiency \approx hardware
flexibility \approx software


Notes:

Conclusions

 ► Example: Field Programmable Gate Arrays (FPGAs).



 - basic idea is that the hardware fabric is reconfigurable, so, in a sense,



- and therefore offers a trade-off:

efficiency \approx hardware
flexibility \approx software

Notes:

Additional Reading

- ▶ *Wikipedia: Hardware Description Language (HDL)*. URL: https://en.wikipedia.org/wiki/Hardware_description_language.
- ▶ *Wikipedia: Verilog*. URL: <https://en.wikipedia.org/wiki/Verilog>.
- ▶ S. Palnitkar. *Verilog HDL: A Guide in Digital Design and Synthesis*. 2nd ed. Prentice Hall, 2003.
- ▶ D. Page. “Chapter 3: Hardware design using Verilog”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009.

Notes:

References

- [1] *Wikipedia: Hardware Description Language (HDL)*. URL: https://en.wikipedia.org/wiki/Hardware_description_language (see p. 125).
- [2] *Wikipedia: Verilog*. URL: <https://en.wikipedia.org/wiki/Verilog> (see p. 125).
- [3] D. Page. “Chapter 3: Hardware design using Verilog”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009 (see p. 125).
- [4] S. Palnitkar. *Verilog HDL: A Guide in Digital Design and Synthesis*. 2nd ed. Prentice Hall, 2003 (see p. 125).

Notes: