

Computer Architecture

Daniel Page

Department of Computer Science,
University Of Bristol,
Merchant Venturers Building,
Woodland Road,
Bristol, BS8 1UB. UK.
(csdsp@bristol.ac.uk)

September 17, 2026

Keep in mind there are *two* PDFs available (of which this is the latter):

1. a PDF of examinable material used as lecture slides, and
2. a PDF of non-examinable, extra material:
 - ▶ the associated notes page may be pre-populated with extra, written explanation of material covered in lecture(s), plus
 - ▶ anything with a “grey’ed out” header/footer represents extra material which is useful and/or interesting but out of scope (and hence not covered).

Notes:

Notes:

- **Agenda:** introduce the topic [4, Part 1] of

finite automata $\equiv$ **Finite State Machines (FSMs)**

via

1. an “in theory”, i.e., concept-oriented perspective, and
2. an “in practice”, i.e., perspective, spanning
 - 2.1 general application, and
 - 2.2 specific implementation in sequential logic design.

Notes:

Part 1: in theory (1)

Definition

An **alphabet** is a non-empty set of **symbols**.

Definition

A **string** X with respect to some alphabet Σ is a sequence, of finite length, whose elements are members of Σ , i.e.,

$$X = \langle X_0, X_1, \dots, X_{n-1} \rangle$$

for some n such that $X_i \in \Sigma$ for $0 \leq i < n$; if n is zero, we term X the **empty string** and denote it ϵ . It can be useful, and is common to write elements in human-readable form termed a **string literal**: this basically means writing them from right-to-left without any associated notation (e.g., brackets or commas).

Definition

A **language** Λ is a set of strings.

Notes:

Definition

A (formal) **grammar** is a tuple

$$G = (N, n, T, P)$$

including

1. N , a finite set of **non-terminal symbols** that includes a **start symbol** $n \in N$,
2. T , a finite set of **terminal symbols** (which is disjoint from N), and
3. P , a finite set of **production rules** each of the form

$$P_i : (N \cup T)^* \rightarrow (N \cup T)^*.$$

Notes:

Part 1: in theory (3)

- **Concept:** **Finite State Machines (FSMs)** are a model of **computation**.

Notes:

Part 1: in theory (3)

- ▶ **Concept: Finite State Machines (FSMs)** are a model of **computation**.
 - ▶ An FSM is an (idealised) computer C , which, at a given point in time, is in one of some finite set of states.

Notes:

Part 1: in theory (3)

- ▶ **Concept: Finite State Machines (FSMs)** are a model of **computation**.
 - ▶ An FSM is an (idealised) computer C , which, at a given point in time, is in one of some finite set of states.
 - ▶ C accepts an input string with respect to some alphabet Σ , one symbol at a time; each symbol potentially induces a change in state.

Notes:

Part 1: in theory (3)

- ▶ **Concept: Finite State Machines (FSMs)** are a model of **computation**.
 - ▶ An FSM is an (idealised) computer C , which, at a given point in time, is in one of some finite set of states.
 - ▶ C accepts an input string with respect to some alphabet Σ , one symbol at a time; each symbol potentially induces a change in state.
 - ▶ Once the input is exhausted, C halts: depending on the state it halts in, we say either
 1. C accepts (or recognises) the input string
 2. C rejects the input string

Notes:

Part 1: in theory (3)

- ▶ **Concept: Finite State Machines (FSMs)** are a model of **computation**.
 - ▶ An FSM is an (idealised) computer C , which, at a given point in time, is in one of some finite set of states.
 - ▶ C accepts an input string with respect to some alphabet Σ , one symbol at a time; each symbol potentially induces a change in state.
 - ▶ Once the input is exhausted, C halts: depending on the state it halts in, we say either
 1. C accepts (or recognises) the input string
 2. C rejects the input string
 - ▶ For a language Λ of all possible input strings C could accept, we say
$$C \text{ accepts (or recognises) } \Lambda \equiv \Lambda \text{ is the language of } C$$
and use Λ to classify C ...

Notes:

Part 1: in theory (4)

Definition

	less powerful more powerful				
Machine	Combinatorial logic	Finite automaton	Push-down automaton	Linear-bounded automaton	Turing machine
Memory		0 stacks	1 stacks	2 stacks	2 stacks
Language		regular	context free	context sensitive	recursively enumerable
Grammar		regular ($X \rightarrow x$ or $X \rightarrow xY$)	context free ($X \rightarrow \gamma$)	context sensitive ($\alpha X \beta \rightarrow \alpha \gamma \beta$)	unrestricted ($\alpha \rightarrow \beta$)
Chomsky-Schützenberger hierarchy		type-3	type-2	type-1	type-0


Notes:

- In the description of grammars, the idea is (read from left-to-right) there are progressively less and less restrictions: X and Y both represent non-terminal symbols, x represents a terminal symbol, and α , β and γ are strings of either terminal or non-terminal symbols, all with respect to some alphabet and grammar. So, the far right-hand case has rules that are totally unrestricted, for example, whereas the far left-hand case has rules that must be of a particular form.

© Daniel Page <csdsp@bristol.ac.uk>
Computer Architecture



Part 1: in theory (5)

 

Notes:

<https://xkcd.com/1195>

© Daniel Page csdsp@bristol.ac.uk
Computer Architecture



Part 1: in theory (6)

Definition

A (deterministic) **Finite State Machine (FSM)** is a tuple

$$C = (S, s, A, \Sigma, \Gamma, \delta, \omega)$$

including

1. S , a finite set of **states** that includes a **start state** $s \in S$,
2. $A \subseteq S$, a finite set of **accepting states**,
3. an **input alphabet** Σ and an **output alphabet** Γ ,
4. a **transition function**

$$\delta : S \times \Sigma \rightarrow S$$

and

5. an **output function**

$$\omega : S \rightarrow \Gamma$$

in the case of a **Moore FSM**, or

$$\omega : S \times \Sigma \rightarrow \Gamma$$

in the case of a **Mealy FSM**,

noting an **empty** input denoted ϵ allows a transition that can *always* occur.

Notes:

- Even if the state space is *huge*, it is still finite: to cope, δ can a **partial function** meaning it needn't be defined for all inputs.


Part 1: in theory (7)

- **Problem:** design an FSM that decides whether a binary sequence X has an odd number of 1 elements in it.

Notes:

Part 1: in theory (7)

► Solution:

 Algorithm (tabular)		Algorithm (diagram)											
<table><tr><th rowspan="2">Q</th><th colspan="2">δ</th></tr><tr><th>Q' $X_i = 0$</th><th>$X_i = 1$</th></tr><tr><td>S_{even}</td><td>S_{even}</td><td>S_{odd}</td></tr><tr><td>S_{odd}</td><td>S_{odd}</td><td>S_{even}</td></tr></table>	Q	δ		Q' $X_i = 0$	$X_i = 1$	S_{even}	S_{even}	S_{odd}	S_{odd}	S_{odd}	S_{even}		
Q		δ											
	Q' $X_i = 0$	$X_i = 1$											
S_{even}	S_{even}	S_{odd}											
S_{odd}	S_{odd}	S_{even}											

where, e.g.,

1. for the input string $X = \langle 1, 0, 1, 1 \rangle$ the transitions are

$\leadsto S_{even} \xrightarrow{X_0=1} S_{odd} \xrightarrow{X_1=0} S_{odd} \xrightarrow{X_2=1} S_{even} \xrightarrow{X_3=1} S_{odd}$

so the input is accepted (i.e., has an odd number of 1 elements).

2. for the input string $X = \langle 0, 1, 1, 0 \rangle$ the transitions are

$\leadsto S_{even} \xrightarrow{X_0=0} S_{even} \xrightarrow{X_1=1} S_{odd} \xrightarrow{X_2=1} S_{even} \xrightarrow{X_3=0} S_{even}$

so the input is rejected (i.e., has an even number of 1 elements).


Notes:

Part 2.1: in practice, application (1)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► Context:

► -ve perspective:

 

► +ve perspective: we could say that

arithmetic expression	$\xrightarrow{\text{evaluate}}$	number
regular expression	$\xrightarrow{\text{evaluate}}$	language

so a regular expression (or regex) can be used as

1. a pattern used to describe or generate a language, *or*
2. a pattern used to identify (i.e., match) members of a language.

Notes:

Definition

We say X is a **regular expression** if it is

1. a symbol in the alphabet, i.e., $\{x\}$ for $x \in \Sigma$,
2. the union of regular expressions X and Y such that
$$X \cup Y = \{x \mid x \in X \vee x \in Y\},$$
3. the concatenation of regular expressions X and Y such that
$$X \parallel Y = \{\langle x, y \rangle \mid x \in X \wedge y \in Y\},$$
or
4. the **Kleene star** of regular expression X such that
$$X^* = \{\langle x_0, x_1, \dots, x_{n-1} \rangle \mid n \geq 0, x_i \in X\}.$$

allowing for various short-hands, e.g.,

x	$\equiv$	$\{x\}$
xy	$\equiv$	$\{x\} \parallel \{y\}$
X^+	$\equiv$	$X \parallel X^*$

Notes:

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$0^*10^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string containing} \\ \text{a single } 1 \end{array} \right\}$$

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking: if the FSM accepts a '1' followed by something other than '0' then it fails, but obviously this ignores the possibility that there might be *another* '1' later which *is* followed by '0'. So the description might be better written as “ s is a line read from `stdin`, where a) there is at least one '1' character, and b) the first '1' character is followed by at least one '0' character”. We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).


Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$0^*10^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string containing} \\ \text{a single } 1 \end{array} \right\}$$

which can be realised using

 

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking; if the FSM accepts a '1' followed by something other than '0' then it fails, but obviously this ignores the possibility that there might be *another* '1' later which is followed by '0'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one '1' character, and b) the first '1' character is followed by at least one '0' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).

Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$\Sigma^*001\Sigma^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string containing} \\ 001 \text{ as a sub-string} \end{array} \right\}$$

which can be realised using

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking; if the FSM accepts a '1' followed by something other than '0' then it fails, but obviously this ignores the possibility that there might be *another* '1' later which is followed by '0'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one '1' character, and b) the first '1' character is followed by at least one '0' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).


Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$\Sigma^*001\Sigma^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string containing} \\ 001 \text{ as a sub-string} \end{array} \right\}$$

which can be realised using

 

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking; if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).

Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$(\Sigma\Sigma)^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string} \\ \text{of even length} \end{array} \right\}$$

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking; if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).


Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$(\Sigma\Sigma)^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string} \\ \text{of even length} \end{array} \right\}$$

which can be realised using

 

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking: if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).

Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$1^*(01^+)^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string in which} \\ \text{every 0 is followed by at least one 1} \end{array} \right\}$$

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking: if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).


Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{0, 1\}$, then

$$1^*(01^+)^* \equiv \left\{ s \mid \begin{array}{l} s \text{ is a string in which} \\ \text{every } 0 \text{ is followed by at least one } 1 \end{array} \right\}$$

which can be realised using

 

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking: if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).

Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{ 'a', 'b', \dots, 'z' \}$, then

$$\text{grep -E '.*to+.*'} \equiv \left\{ s \mid \begin{array}{l} s \text{ is a line read from } \text{stdin} \text{ containing} \\ \text{a 't' followed by at least one 'o' character} \end{array} \right\}$$

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking: if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).


Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{ 'a', 'b', \dots, 'z' \}$, then

$$\text{grep -E '.*to+.*'} \equiv \left\{ s \mid \begin{array}{l} s \text{ is a line read from stdin containing} \\ \text{a 't' followed by at least one 'o' character} \end{array} \right\}$$

 which can be (sort of, with a significant caveat) realised using



Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking: if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).

Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{ 'a', 'b', \dots, 'z' \}$, then

$$\text{grep -E '.*to+.*'} \equiv \left\{ s \mid \begin{array}{l} s \text{ is a line read from stdin containing} \\ \text{a 't' followed by at least one 'o' character} \end{array} \right\}$$

which can be (sort of, with a significant caveat) realised using

```
1 forall lines X read from stdin do
3   Q ← s
4   for i = 0 upto n - 1 do
5     | Q ← δ(Q, Xi)
6   end
7   if Q ∈ A then
8     | print line X to stdout
9   end
10 end
11 end
```

Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking: if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).

Part 2.1: in practice, application (3)

Example #1: regular expressions + `grep` $\leadsto$ FSMs as recognisers

► **Example** [4, Example 1.53]: if $\Sigma = \{ 'a', 'b', \dots, 'z' \}$, then

`grep -E '.*to+.*'` $\equiv \left\{ s \mid \begin{array}{l} s \text{ is a line read from stdin containing} \\ \text{a 't' followed by at least one 'o' character} \end{array} \right\}$

which can be (sort of, with a significant caveat) realised using

```
1 void grep() {
2   char X[ 1024 ];
3
4   while( NULL != fgets( X, 1024, stdin ) ) {
5     int n = strlen( X ), Q = start;
6
7     if( X[ n - 1 ] == '\n' ) {
8       X[ n - 1 ] = '\0'; n--;
9     }
10
11    for( int i = 0; i < n; i++ ) {
12      Q = delta[ Q ][ X[ i ] ];
13    }
14
15    if( accept[ Q ] ) {
16      fprintf( stdout, "%s\n", X );
17    }
18  }
19 }
```


Notes:

- The example implementation in the `grep` example is a little simplistic, so the behaviour (and hence output) will differ versus use of `grep` itself. The technical reason for this is that we have ignored (or disallowed) backtracking; if the FSM accepts a 't' followed by something other than 'o' then it fails, but obviously this ignores the possibility that there might be *another* 't' later which is followed by 'o'. So the description might be better written as "s is a line read from `stdin`, where a) there is at least one 't' character, and b) the first 't' character is followed by at least one 'o' character". We could try to capture that using a more complex transition function, but then the example becomes overly complex: although the details is important in a general sense, the underlying idea is more important at this point. In *even* more detail, the difference here relates to a difference between so-called Deterministic Finite Automatons (DFAs) and Non-deterministic Finite Automatons (NFAs): we are dealing with and assume the former, whereas `grep` makes use of the latter (see, e.g., [4, Section 1.2]).

Part 2.1: in practice, application (4)


Example #2: networked communication via TCP $\leadsto$ FSMs as controllers

► **Context:**

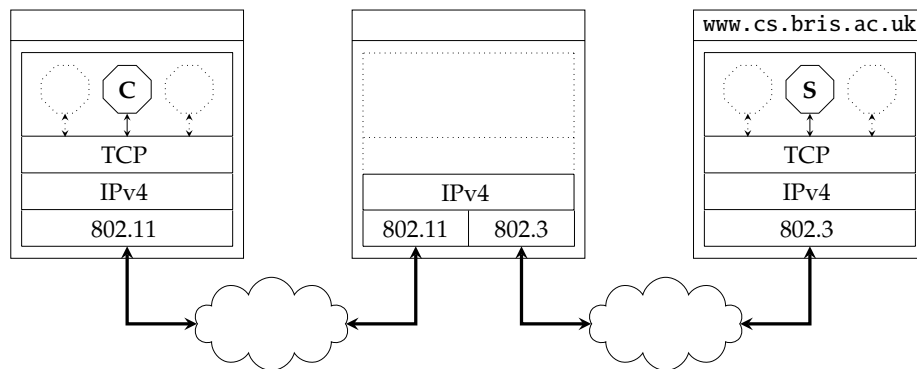

Notes:

► Example:

 

Notes:

► Context:



Algorithm

```
1 reset the game state
2 while  $\neg$  game over do
3   read control pad (e.g., check if button pressed)
4   update game state (e.g., move player)
5   produce graphics and/or sound
6 end
```

Notes:

► Context:



Algorithm

```


1  $Q \leftarrow s$ 
2 while  $Q \notin A$  do
3    $X_i \leftarrow$  control pad
4    $Q \leftarrow \delta(Q, X_i)$ 
5    $\{\text{graphics, sound}\} \leftarrow \omega(Q)$ 
6 end
    
```

Notes:

► Example:

iterations of game loop $\leadsto$ game tree
 $\simeq$ state space

i.e.,

 

which is most obvious with respect to turn-based games (e.g., chess).

Notes:

► Recall:

Definition

A (deterministic) **Finite State Machine (FSM)** is a tuple

$$C = (S, s, A, \Sigma, \Gamma, \delta, \omega)$$

including

1. S , a finite set of **states** that includes a **start state** $s \in S$,
2. $A \subseteq S$, a finite set of **accepting states**,
3. an **input alphabet** Σ and an **output alphabet** Γ ,
4. a **transition function**

$$\delta : S \times \Sigma \rightarrow S$$

and

5. an **output function**

$$\omega : S \rightarrow \Gamma$$

in the case of a **Moore FSM**, or

$$\omega : S \times \Sigma \rightarrow \Gamma$$


in the case of a **Mealy FSM**,

noting an **empty** input denoted ϵ allows a transition that can *always* occur.

Notes:

► Concept:

Algorithm (latch version)

 

► Note that


1. the state is retained in a register (i.e., a group of latches, resp. flip-flops),
2. δ and ω are simply combinatorial logic,
3. within the current clock cycle
 - ω computes the output from the current state and input, and
 - δ computes the next state from the current state and input,
4. the next state is latched by an appropriate feature (i.e., level, resp. edge) in the clock

i.e., it's a *computer* we can *build*!

Notes:

► Concept:

Algorithm (flip-flop version)

 

► Note that


1. the state is retained in a register (i.e., a group of latches, resp. flip-flops),
2. δ and ω are simply combinatorial logic,
3. within the current clock cycle
 - ω computes the output from the current state and input, and
 - δ computes the next state from the current state and input,
4. the next state is latched by an appropriate feature (i.e., level, resp. edge) in the clock

i.e., it's a *computer* we can *build*!

Notes:

► Concept:

 
Example (latch version: input $X = \langle X_0, X_1, \dots \rangle$, output $Y = \langle Y_0, Y_1, \dots \rangle$)



Notes:

► Concept:

 
Example (flip-flop version: input $X = \langle X_0, X_1, \dots \rangle$, output $Y = \langle Y_0, Y_1, \dots \rangle$)



Notes:

► Concept: this *should* sound familiar, because from

Circuit (latch version)

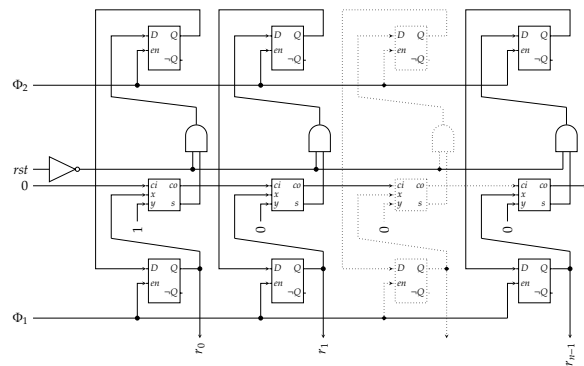


it *now* becomes clear that

- 2^n states, labelled S_0 through S_{2^n-1} ; state S_i represented as (unsigned) n -bit integer i ,
- the start state is $s = S_0$ and there are no accepting states (so $A = \emptyset$),

Notes:

- **Concept:** this *should* sound familiar, because from

Circuit (latch version)

 

it *now* becomes clear that


- the δ function is

$$Q' \leftarrow \delta(Q, rst) = \begin{cases} Q + 1 \pmod{2^n} & \text{if } rst = 0 \\ 0 & \text{if } rst = 1 \end{cases}$$

Notes:

- **Concept:** this *should* sound familiar, because from

Circuit (latch version)

 


it *now* becomes clear that

- the ω function is $r \leftarrow \omega(Q) = Q$.

Notes:

- **Concept:** this *should* sound familiar, because from

Circuit (flip-flop version)

 


it *now* becomes clear that

- 2^n states, labelled S_0 through S_{2^n-1} ; state S_i represented as (unsigned) n -bit integer i ,
- the start state is $s = S_0$ and there are no accepting states (so $A = \emptyset$),

Notes:

- **Concept:** this *should* sound familiar, because from

Circuit (flip-flop version)

 

it *now* becomes clear that


- the δ function is

$$Q' \leftarrow \delta(Q, rst) = \begin{cases} Q + 1 & (\text{mod } 2^n) & \text{if } rst = 0 \\ 0 & \text{if } rst = 1 \end{cases}$$

Notes:

- **Concept:** this *should* sound familiar, because from

Circuit (flip-flop version)

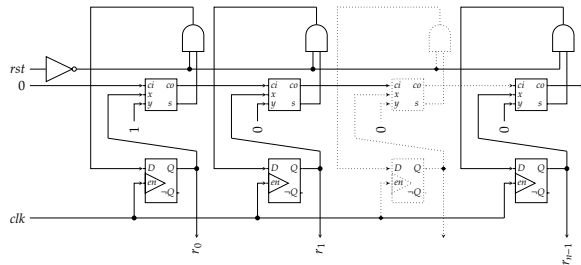

it *now* becomes clear that

- the ω function is $r \leftarrow \omega(Q) = Q$.

Notes:

- **Concept:** to solve a concrete problem, we follow a (fairly) standard sequence of steps

Algorithm

1. Count the number of states required, and give each state an abstract label.
2. Describe the state transition and output functions using a tabular or diagrammatic approach.
3. Perform state assignment, i.e., decide how concrete values will represent the abstract labels, allocating appropriate register(s) to hold the state.
4. Express the functions δ and ω as (optimised) Boolean expressions, i.e., combinatorial logic.
5. Place the registers and combinatorial logic into the framework.

noting that it's common to

- include a **reset** input that (re)initialises the FSM into the start state,
- replace the accepting state(s) with an **idle** or **error** state since "halting" doesn't make sense in hardware, and
- use the FSM to control an associated data-path using the outputs, rather than (necessarily) solve some problem outright.

Notes:

► **Concept:** we can optimise the state representation based on use of it, e.g.,

1. a **binary encoding** represents the i -th of n states as a $(\lceil \log_2(n) \rceil)$ -bit unsigned integer i , e.g.,

S_0	$\mapsto$	$\langle 0, 0, 0 \rangle$
S_1	$\mapsto$	$\langle 1, 0, 0 \rangle$
S_2	$\mapsto$	$\langle 0, 1, 0 \rangle$
S_3	$\mapsto$	$\langle 1, 1, 0 \rangle$
S_4	$\mapsto$	$\langle 0, 0, 1 \rangle$
S_5	$\mapsto$	$\langle 1, 0, 1 \rangle$

2. a **one-hot encoding** represents the i -th of n states as a sequence X such that $X_i = 1$ and $X_j = 0$ for $j \neq i$, e.g.,

S_0	$\mapsto$	$\langle 1, 0, 0, 0, 0, 0 \rangle$
S_1	$\mapsto$	$\langle 0, 1, 0, 0, 0, 0 \rangle$
S_2	$\mapsto$	$\langle 0, 0, 1, 0, 0, 0 \rangle$
S_3	$\mapsto$	$\langle 0, 0, 0, 1, 0, 0 \rangle$
S_4	$\mapsto$	$\langle 0, 0, 0, 0, 1, 0 \rangle$
S_5	$\mapsto$	$\langle 0, 0, 0, 0, 0, 1 \rangle$

noting that we have a larger state (i.e., n bits instead of $\lceil \log_2(n) \rceil$), *but*

- transition between states is easier, *and*
- switching behaviour (and hence power consumption) is reduced.

Notes:

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► **Problem:** design an FSM that acts as a cyclic counter modulo $n = 6$ (versus 2^n).

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values

$0, 1, 2, 3, 4, 5, 0, 1, \dots,$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)


Example #1: a modulo 6 ascending counter

► Solution:

Algorithm (tabular)

	δ	ω
Q	Q'	r
S_0	S_1	0
S_1	S_2	1
S_2	S_3	2
S_3	S_4	3
S_4	S_5	4
S_5	S_0	5

Algorithm (diagram)

 

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values

$0, 1, 2, 3, 4, 5, 0, 1, \dots,$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► Solution:

- there are 6 abstract labels

$S_0 \mapsto 0$
 $S_1 \mapsto 1$
 $S_2 \mapsto 2$
 $S_3 \mapsto 3$
 $S_4 \mapsto 4$
 $S_5 \mapsto 5$

we can represent using 6 concrete values, e.g.,

$S_0 \mapsto \langle 0, 0, 0 \rangle \equiv 000_{(2)}$
 $S_1 \mapsto \langle 1, 0, 0 \rangle \equiv 001_{(2)}$
 $S_2 \mapsto \langle 0, 1, 0 \rangle \equiv 010_{(2)}$
 $S_3 \mapsto \langle 1, 1, 0 \rangle \equiv 011_{(2)}$
 $S_4 \mapsto \langle 0, 0, 1 \rangle \equiv 100_{(2)}$
 $S_5 \mapsto \langle 1, 0, 1 \rangle \equiv 101_{(2)}$

- since $2^3 = 8 > 6$, we can capture each of

1. $Q = \langle Q_0, Q_1, Q_2 \rangle \equiv$ the current state
2. $Q' = \langle Q'_0, Q'_1, Q'_2 \rangle \equiv$ the next state

in a 3-bit register (i.e., via 3 latches or flip-flops).

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values

$0, 1, 2, 3, 4, 5, 0, 1, \dots,$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► Solution:

- rewriting the abstract labels yields the following concrete truth table

			δ			ω		
Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	r_2	r_1	r_0
0	0	0	0	0	1	0	0	0
0	0	1	0	1	0	0	0	1
0	1	0	0	1	1	0	1	0
0	1	1	1	0	0	0	1	1
1	0	0	1	0	1	1	0	0
1	0	1	0	0	0	1	0	1
1	1	0	?	?	?	?	?	?
1	1	1	?	?	?	?	?	?

- note that our state assignment means $r = Q$, such that

$$r = \omega(Q) = Q$$

is basically just the identity function (so we'll ignore it).

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values

$$0, 1, 2, 3, 4, 5, 0, 1, \dots,$$


with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► Solution:

- the truth table can be translated into

 

- doing so yields the following Boolean expressions for δ :

$$Q'_2 = (\quad \quad \quad Q_1 \quad \wedge \quad Q_0 \quad) \vee (\quad Q_2 \quad \wedge \quad \quad \neg Q_0 \quad)$$

$$Q'_1 = (\quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad Q_0 \quad) \vee (\quad \quad \quad Q_1 \quad \wedge \quad \neg Q_0 \quad)$$

$$Q'_0 = (\quad \quad \quad \neg Q_0 \quad)$$

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values


$$0, 1, 2, 3, 4, 5, 0, 1, \dots,$$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► Solution:

 

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values


$0, 1, 2, 3, 4, 5, 0, 1, \dots,$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► Solution:

 

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values


$0, 1, 2, 3, 4, 5, 0, 1, \dots,$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► Solution:

 

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values


$0, 1, 2, 3, 4, 5, 0, 1, \dots,$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (10)

Example #1: a modulo 6 ascending counter

► Solution:

 

Notes:

- If $n = 6$ for example, then we want a component whose output r steps through values

$0, 1, 2, 3, 4, 5, 0, 1, \dots,$

with the modular reduction representing control behaviour (versus the uncontrolled counter that was cyclic by default).

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Problem: design an FSM that

1. acts as a cyclic counter modulo $n = 6$ (versus 2^n),
2. has an input d which selects between increment and decrement, and
3. has an output f which signals when a cycle occurs.

Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)


Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Solution:

Algorithm (tabular)

Q	δ		r	ω	
	$d = 0$	$d = 1$		$d = 0$	$d = 1$
S_0	S_1	S_5	0	0	1
S_1	S_2	S_0	1	0	0
S_2	S_3	S_1	2	0	0
S_3	S_4	S_2	3	0	0
S_4	S_5	S_3	4	0	0
S_5	S_0	S_4	5	1	0

Algorithm (diagram)

 

Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Solution:

- there are 6 abstract labels

$$\begin{array}{ll} S_0 & \mapsto 0 \\ S_1 & \mapsto 1 \\ S_2 & \mapsto 2 \\ S_3 & \mapsto 3 \\ S_4 & \mapsto 4 \\ S_5 & \mapsto 5 \end{array}$$

we can represent using 6 concrete values, e.g.,

$$\begin{array}{llll} S_0 & \mapsto & \langle 0, 0, 0 \rangle & \equiv 000_{(2)} \\ S_1 & \mapsto & \langle 1, 0, 0 \rangle & \equiv 001_{(2)} \\ S_2 & \mapsto & \langle 0, 1, 0 \rangle & \equiv 010_{(2)} \\ S_3 & \mapsto & \langle 1, 1, 0 \rangle & \equiv 011_{(2)} \\ S_4 & \mapsto & \langle 0, 0, 1 \rangle & \equiv 100_{(2)} \\ S_5 & \mapsto & \langle 1, 0, 1 \rangle & \equiv 101_{(2)} \end{array}$$

- since $2^3 = 8 > 6$, we can capture each of

1. $Q = \langle Q_0, Q_1, Q_2 \rangle \equiv$ the current state
2. $Q' = \langle Q'_0, Q'_1, Q'_2 \rangle \equiv$ the next state

in a 3-bit register (i.e., via 3 latches or flip-flops).

Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Solution:

- rewriting the abstract labels yields the following concrete truth table

				δ			ω			
d	Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	r_2	r_1	r_0	f
0	0	0	0	0	0	1	0	0	0	0
0	0	0	1	0	1	0	0	0	1	0
0	0	1	0	0	1	1	0	1	0	0
0	0	1	1	1	0	0	0	1	1	0
0	1	0	0	1	0	1	1	0	0	0
0	1	0	1	0	0	0	1	0	1	1
0	1	1	0	?	?	?	?	?	?	?
0	1	1	1	?	?	?	?	?	?	?
1	0	0	0	1	0	1	0	0	0	1
1	0	0	1	0	0	0	0	0	1	0
1	0	1	0	0	0	1	0	1	0	0
1	0	1	1	0	1	0	0	1	1	0
1	1	0	0	0	1	1	1	0	0	0
1	1	0	1	1	0	0	1	0	1	0
1	1	1	0	?	?	?	?	?	?	?
1	1	1	1	?	?	?	?	?	?	?

Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* decending counter, with cycle alert

► Solution:

- the truth table can be translated into

Q_2	Q_1	Q_2'
00	00	0
00	01	0
00	11	1
00	10	0
01	00	1
01	01	0
01	11	?
01	10	?
11	00	0
11	01	1
11	11	?
11	10	?
10	00	1
10	01	0
10	11	0
10	10	0

Q_2	Q_1	Q_1'
00	00	0
00	01	1
00	11	0
00	10	1
01	00	0
01	01	0
01	11	?
01	10	?
11	00	1
11	01	0
11	11	?
11	10	?
10	00	0
10	01	0
10	11	1
10	10	0

Q_2	Q_1	Q_0'
00	00	1
00	01	0
00	11	0
00	10	1
01	00	1
01	01	0
01	11	?
01	10	?
11	00	1
11	01	0
11	11	?
11	10	?
10	00	1
10	01	0
10	11	0
10	10	1

- doing so yields the following Boolean expressions for δ :

$$Q_2' = (\neg d \quad \quad \quad \wedge \quad Q_1 \quad \wedge \quad Q_0) \vee \\ (\neg d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad \neg Q_0) \vee \\ (\quad d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad Q_0) \vee \\ (\quad d \quad \wedge \quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad \neg Q_0)$$

$$Q_1' = (\neg d \quad \wedge \quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad Q_0) \vee \\ (\neg d \quad \quad \quad \wedge \quad Q_1 \quad \wedge \quad \neg Q_0) \vee \\ (\quad d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad \neg Q_0) \vee \\ (\quad d \quad \quad \quad \wedge \quad Q_1 \quad \wedge \quad Q_0)$$

$$Q_0' = (\quad \quad \quad \neg Q_0)$$

Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* decending counter, with cycle alert

► Solution:

- the truth table can be translated into

Q_2	Q_1	f
00	00	0
00	01	0
00	11	0
00	10	0
01	00	0
01	01	1
01	11	?
01	10	?
11	00	0
11	01	0
11	11	?
11	10	?
10	00	1
10	01	0
10	11	0
10	10	0

- doing so yields the following Boolean expressions for ω :

$$f = (\neg d \quad \wedge \quad Q_2 \quad \quad \quad \wedge \quad Q_0) \vee \\ (\quad d \quad \wedge \quad \neg Q_2 \quad \wedge \quad \neg Q_1 \quad \wedge \quad \neg Q_0)$$


Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Solution:

 


Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Solution:

 


Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Solution:

 


Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (11)

Example #2: a modulo 6 ascending *or* descending counter, with cycle alert

► Solution:

 

Notes:

- If $n = 6$, for example, then
 - if $d = 0$
 - the output r steps through values 0, 1, 2, 3, 4, 5, 0, 1, ...
 - the output $f = 1$ iff. $r = 5$
 - if $d = 1$
 - the output r steps through values 0, 5, 4, 3, 2, 1, 0, 5, ...
 - the output $f = 1$ iff. $r = 0$.

Part 2.2: in practice, implementation (12)

Example #3: a loop counter

► Problem: design an FSM that

- replicates the behaviour of a controlled loop counter, e.g., `i` within a C-style for loop such as

```
for( int i = m; i < n; i++ ) {  
    ...  
}
```

- has an interface that allows signalling for

the start of iteration $\equiv$ so $i = m$
the end of iteration $\equiv$ when $i = n$

focused wlog. on 4-bit values of i , m , and n .

Notes:

Part 2.2: in practice, implementation (13)

Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 - uses a shared clock signal to synchronise events,
 - uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 - ...

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 - When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 - When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

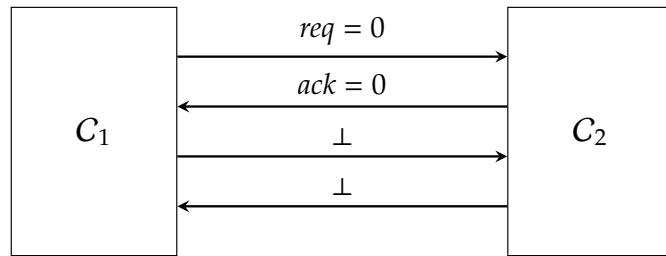

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

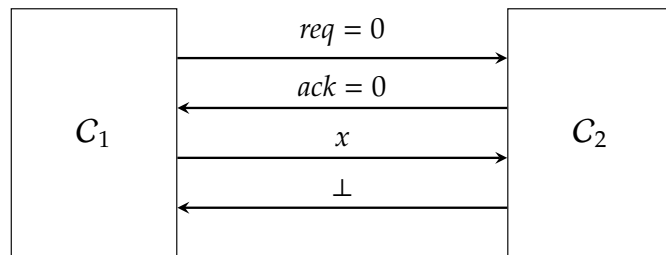

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

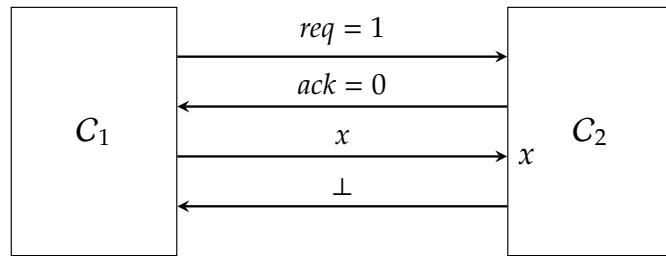

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:

- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, $req = 0$ and $ack = 0$.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing req from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) req and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing ack from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) ack and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing req from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) req and concludes that the interaction is finished. It proceeds by changing ack from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) ack and concludes that the interaction is finished.
 - Since both req and ack are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (13)


Example #3: a loop counter

► Design:

- given a user C_1 of some component C_2 , how does
 - C_2 know when to start computation (e.g., when any input x is available), and
 - C_1 know when computation has finished (e.g., when any output $r = f(x)$ is available).
- we could implement an the interface which
 1. uses a shared clock signal to synchronise events,
 2. uses a **control protocol**, e.g., via additional *req* (or **request**) and *ack* (or **acknowledge**) signals,
 3. ...

► Example:

Algorithm

 

Notes:


- A shared clock might *seem* the ideal option, but there are (at least) two scenarios where it doesn't work out so well:
 1. When C_2 and C_1 are physically separate: distribution of a synchronised clock will be significantly hard(er). and
 2. When the number of steps C_2 takes is variable: even if C_2 and C_1 are synchronised, the latter still needs some way to tell when the former has completed a given computation.
- The diagrammatic example can be explained as follows:
 - Initially, *req* = 0 and *ack* = 0.
 - At some point, C_1 wants to start a computation. It proceeds by 1) driving values onto any inputs (e.g., x) then 2) changing *req* from 0 to 1.
 - C_2 notices the change to (e.g., positive edge on) *req* and concludes that the inputs are available.
 - C_2 computes the outputs from the inputs (e.g., $r = f(x)$).
 - At some point, C_2 finishes the computation. It proceeds by 1) driving values onto any outputs (e.g., r) then 2) changing *ack* from 0 to 1.
 - C_1 notices the change to (e.g., positive edge on) *ack* and concludes that the outputs are available. It proceeds by 1) storing any outputs ready for subsequent use, then 2) changing *req* from 1 to 0.
 - C_2 notices the change to (e.g., negative edge on) *req* and concludes that the interaction is finished. It proceeds by changing *ack* from 1 to 0.
 - C_1 notices the change to (e.g., negative edge on) *ack* and concludes that the interaction is finished.
 - Since both *req* and *ack* are 0 again, the module and user are ready to engage in successive interactions if/when need be.

Part 2.2: in practice, implementation (14)

Example #3: a loop counter

► Design:

Circuit (latch version)

 

i.e., the design is *itself* the combination of

- a **data-path**, of computational and/or storage components, and
- a **control-path**, that tells components in the data-path what to do and when to do it, with the latter more overtly realised using an FSM.


Notes:

Part 2.2: in practice, implementation (14)

Example #3: a loop counter

► Design:

Circuit (flip-flop version)

 

i.e., the design is *itself* the combination of

- a **data-path**, of computational and/or storage components, and
- a **control-path**, that tells components in the data-path what to do and when to do it, with the latter more overtly realised using an FSM.


Notes:

Part 2.2: in practice, implementation (15)

Example #3: a loop counter

► Solution: the data-path.

Circuit (latch version)

 

Notes:

- The general structure here is the same as the previous, uncontrolled counter example: for example there is 1) there is still a register to store the current counter state, 2) there is still have an adder, but 3) there is *also* now a multiplexer to decide between several options for the next state.
- Some of the inputs (e.g., Q) and outputs (e.g., cmp) shown need to be considered in combination with the control-path. For example, it should now be clear that
 - if $Q = (0, 0) \mapsto S_{init}$, then the multiplexer updates the output register with 0,
 - if $Q = (1, 0) \mapsto S_{init}$ then the multiplexer updates the output register with m , i.e., the initial counter value,
 - if $Q = (0, 1) \mapsto S_{step}$ then the multiplexer updates the output register with $i + 1$, i.e., the incremented counter value produced by the adder,
 - if $Q = (1, 1) \mapsto S_{done}$ then the multiplexer updates the output register with i , i.e., the current counter value.

Likewise, it should be clear that

$$cmp = \begin{cases} 0 & \text{if } i < n \\ 1 & \text{if } i \geq n \end{cases}$$


which controls the transition from S_{step} into S_{done} .

Part 2.2: in practice, implementation (15)

Example #3: a loop counter

► **Solution:** the data-path.

Circuit (flip-flop version)

 

Notes:

- The general structure here is the same as the previous, uncontrolled counter example: for example there is 1) there is still a register to store the current counter state, 2) there is still have an adder, but 3) there is *also* now a multiplexer to decide between several options for the next state.
- Some of the inputs (e.g., Q) and outputs (e.g., cmp) shown need to be considered in combination with the control-path. For example, it should now be clear that
 - if $Q = (0, 0) \mapsto S_{wait}$, then the multiplexer updates the output register with 0,
 - if $Q = (1, 0) \mapsto S_{init}$ then the multiplexer updates the output register with m , i.e., the initial counter value,
 - if $Q = (0, 1) \mapsto S_{step}$ then the multiplexer updates the output register with $i + 1$, i.e., the incremented counter value produced by the adder,
 - if $Q = (1, 1) \mapsto S_{done}$ then the multiplexer updates the output register with i , i.e., the current counter value.

Likewise, it should be clear that

$$cmp = \begin{cases} 0 & \text{if } i < n \\ 1 & \text{if } i \geq n \end{cases}$$

which controls the transition from S_{step} into S_{done} .

Part 2.2: in practice, implementation (16)


Example #3: a loop counter

► **Solution:** the control-path.

Algorithm (tabular)

	Q	δ		ω	
		$cmp = 0$	$cmp = 1$	$cmp = 0$	$cmp = 1$
$req = 0$	S_{wait}	S_{wait}	S_{wait}	0	0
	S_{init}	S_{wait}	S_{wait}	0	0
	S_{step}	S_{wait}	S_{wait}	0	0
	S_{done}	S_{wait}	S_{wait}	1	1
$req = 1$	S_{wait}	S_{init}	S_{init}	0	0
	S_{init}	S_{step}	S_{step}	0	0
	S_{step}	S_{done}	S_{step}	0	0
	S_{done}	S_{done}	S_{done}	1	1

Algorithm (diagram)

 

i.e.,

- in S_{wait} it waits for $req = 1$,
- in S_{init} it uses any input to initialise itself (e.g., setting the initial loop counter value),
- in S_{step} it performs an iteration of the loop, and
- in S_{done} it waits for $req = 0$ while setting $ack = 1$.

Notes:

Part 2.2: in practice, implementation (16)

Example #3: a loop counter

► Solution: the control-path.

- there are 4 abstract labels

$$\begin{array}{ll} S_{wait} & \mapsto 0 \\ S_{init} & \mapsto 1 \\ S_{step} & \mapsto 2 \\ S_{done} & \mapsto 3 \end{array}$$

we can represent using 4 concrete values, e.g.,

$$\begin{array}{llll} S_{wait} & \mapsto & \langle 0, 0 \rangle & \equiv 00_{(2)} \\ S_{init} & \mapsto & \langle 1, 0 \rangle & \equiv 01_{(2)} \\ S_{step} & \mapsto & \langle 0, 1 \rangle & \equiv 10_{(2)} \\ S_{done} & \mapsto & \langle 1, 1 \rangle & \equiv 11_{(2)} \end{array}$$

- since $2^2 = 4$, we can capture each of

1. $Q = \langle Q_0, Q_1 \rangle \equiv$ the current state
2. $Q' = \langle Q'_0, Q'_1 \rangle \equiv$ the next state

in a 2-bit register (i.e., via 2 latches or flip-flops).

Notes:

Part 2.2: in practice, implementation (16)

Example #3: a loop counter

► Solution: the control-path.

- rewriting the abstract labels yields the following concrete truth table

				δ		ω
<i>req</i>	<i>cmp</i>	Q_1	Q_0	Q'_1	Q'_0	<i>ack</i>
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	0	1	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	1	1

Notes:

Part 2.2: in practice, implementation (16)

Example #3: a loop counter

- **Solution:** the control-path.
 - the truth table can be translated into

		Q_1			
		Q_0			
		00	01	11	10
Q'_1	00	0	0	0	0
	01	0	0	0	0
	11	0	1	1	1
	10	0	1	1	1
		0	1	1	0
		Q_1			
		Q_0			
		00	01	11	10
Q'_0	00	0	0	0	0
	01	0	0	0	0
	11	1	0	1	0
	10	1	0	1	1
		0	1	1	0

- doing so yields the following Boolean expressions for δ :

$$Q'_1 = (\text{req} \quad \quad \quad \wedge \quad Q_0) \vee (\text{req} \quad \quad \quad \wedge \quad Q_1)$$

$$Q'_0 = (\text{req} \quad \quad \quad \wedge \quad \neg Q_1 \wedge \neg Q_0) \vee (\text{req} \quad \quad \quad \wedge \quad Q_1 \wedge \quad Q_0) \vee (\text{req} \wedge \neg \text{cmp} \wedge \quad Q_1)$$

Notes:

Part 2.2: in practice, implementation (16)

Example #3: a loop counter

- **Solution:** the control-path.
 - the truth table can be translated into

		Q_1			
		Q_0			
		00	01	11	10
ack	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	0
		0	1	1	0
		Q_1			
		Q_0			
		00	01	11	10
ack	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	0
		0	1	1	0

- doing so yields the following Boolean expressions for ω :

$$ack = Q_1 \wedge Q_0$$

Notes:

Part 2.2: in practice, implementation (17)

Example #3: a loop counter

► Use-case:

- we want(ed) to implement a bit-serial multiplier, i.e.,

Algorithm	Circuit
Input: Two unsigned, n-bit, base-2 integers x and y Output: An unsigned, $2n$-bit, base-2 integer $r = y \cdot x$ <pre> 1 $r \leftarrow 0$ 2 for $i = n - 1$ downto 0 step -1 do 3 $r \leftarrow 2 \cdot r$ 4 if $y_i = 1$ then 5 $r \leftarrow r + x$ 6 end 7 end 8 return r </pre>	

- we *did* have the data-path,
- we *didn't* have the control-path.


Notes:

Part 2.2: in practice, implementation (18)

 Example #3: a loop counter

► Use-case:

- we now have the loop counter implemented, i.e.



- the remaining challenge is integration, e.g., specifying
 - any additional data-path components required, and
 - how loop counter (the control-path) controls them
 so we end up with a bit-serial multiplier.

Notes:


Part 2.2: in practice, implementation (18)

Example #3: a loop counter

► Use-case:

- we now have the loop counter implemented, i.e.

Circuit (flip-flop version)

 

- the remaining challenge is integration, e.g., specifying
 - any additional data-path components required, and
 - how loop counter (the control-path) controls them
- so we end up with a bit-serial multiplier.

Notes:

Part 2.2: in practice, implementation (19)

Example #4: a traffic light controller

- **Problem:** design an FSM that controls two sets of UK-style traffic lights:
 - the traffic lights at the intersection is between a main road and an access road,
 - they should stop cars crashing into each other, displaying
 - green on main road and red on access road, then
 - amber on main road and red on access road, then
 - red on main road and amber on access road, then
 - red on main road and green on access road, then
 - red on main road and amber on access road, then
 - amber on main road and red on access road,
 - and then cycle, and
 - they should allow use of an emergency stop button, which
 - forces red on both main and access roads while pushed, then
 - reset the system into an initial start state when released.


Notes:

► Solution:

Algorithm (tabular)

Q	δ		ω					
	Q'							
	$rst = 0$	$rst = 1$	M_g	M_d	M_r	A_g	A_d	A_r
S_0	S_1	S_6	1	0	0	0	0	1
S_1	S_2	S_6	0	1	0	0	0	1
S_2	S_3	S_6	0	0	1	0	1	0
S_3	S_4	S_6	0	0	1	1	0	0
S_4	S_5	S_6	0	0	1	0	1	0
S_5	S_0	S_6	0	1	0	0	0	1
S_6	S_0	S_6	0	0	1	0	0	1

Algorithm (diagram)

 

Notes:

► Solution:

- there are 7 abstract labels

S_0	$\mapsto$	0
S_1	$\mapsto$	1
S_2	$\mapsto$	2
S_3	$\mapsto$	3
S_4	$\mapsto$	4
S_5	$\mapsto$	5
S_6	$\mapsto$	6

we can represent using 7 concrete values, e.g.,

S_0	$\mapsto$	$\langle 0, 0, 0 \rangle$	$\equiv$	$000_{(2)}$
S_1	$\mapsto$	$\langle 1, 0, 0 \rangle$	$\equiv$	$001_{(2)}$
S_2	$\mapsto$	$\langle 0, 1, 0 \rangle$	$\equiv$	$010_{(2)}$
S_3	$\mapsto$	$\langle 1, 1, 0 \rangle$	$\equiv$	$011_{(2)}$
S_4	$\mapsto$	$\langle 0, 0, 1 \rangle$	$\equiv$	$100_{(2)}$
S_5	$\mapsto$	$\langle 1, 0, 1 \rangle$	$\equiv$	$101_{(2)}$
S_6	$\mapsto$	$\langle 0, 1, 1 \rangle$	$\equiv$	$110_{(2)}$

- since
- $2^3 = 8 > 7$
- , we can capture each of

1. $Q = \langle Q_0, Q_1, Q_2 \rangle \equiv$ the current state
2. $Q' = \langle Q'_0, Q'_1, Q'_2 \rangle \equiv$ the next state

in a 3-bit register (i.e., via 3 latches or flip-flops).

Notes:

Part 2.2: in practice, implementation (19)

Example #4: a traffic light controller

► Solution:

- rewriting the abstract labels yields the following concrete truth table

				δ			ω					
rst	Q_2	Q_1	Q_0	Q'_2	Q'_1	Q'_0	M_g	M_a	M_r	A_g	A_a	A_r
0	0	0	0	0	0	1	1	0	0	0	0	1
0	0	0	1	0	1	0	0	1	0	0	0	1
0	0	1	0	0	1	1	0	0	1	0	1	0
0	0	1	1	1	0	0	0	0	1	1	0	0
0	1	0	0	1	0	1	0	0	1	0	1	0
0	1	0	1	0	0	0	0	1	0	0	0	1
0	1	1	0	0	0	0	0	0	1	0	0	1
0	1	1	1	?	?	?	?	?	?	?	?	?
1	0	0	0	1	1	0	1	0	0	0	0	1
1	0	0	1	1	1	0	0	1	0	0	0	1
1	0	1	0	1	1	0	0	0	1	0	1	0
1	0	1	1	1	1	0	0	0	1	1	0	0
1	1	0	0	1	1	0	0	0	1	0	1	0
1	1	0	1	1	1	0	0	1	0	0	0	1
1	1	1	0	1	1	0	0	0	1	0	0	1
1	1	1	1	?	?	?	?	?	?	?	?	?


Notes:

Part 2.2: in practice, implementation (19)

Example #4: a traffic light controller

► Solution:

- the truth table can be translated into

 

- doing so yields the following Boolean expressions for δ :

$$Q'_2 = (rst \vee (Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \vee (Q_1 \wedge Q_0))$$

$$Q'_1 = (rst \vee (\neg Q_2 \wedge \neg Q_1 \wedge Q_0) \vee (\neg Q_2 \wedge Q_1 \wedge \neg Q_0))$$

$$Q'_0 = (\neg rst \wedge \neg Q_1 \wedge \neg Q_0) \vee (\neg rst \wedge \neg Q_2 \wedge \neg Q_0)$$

Notes:

Solution:

- the truth table can be translated into

		Q_1		Q_0	
		00	01	11	10
M_g	Q_2	0	1	0	0
	1	0	0	?	0

		Q_1		Q_0	
		00	01	11	10
M_a	Q_2	0	0	1	0
	1	0	1	?	0

		Q_1		Q_0	
		00	01	11	10
M_r	Q_2	0	0	0	1
	1	1	0	?	1

		Q_1		Q_0	
		00	01	11	10
A_g	Q_2	0	0	0	1
	1	0	0	?	0

		Q_1		Q_0	
		00	01	11	10
A_a	Q_2	0	0	0	1
	1	1	0	?	0

		Q_1		Q_0	
		00	01	11	10
A_r	Q_2	0	1	1	0
	1	0	1	?	1

- doing so yields the following Boolean expressions for δ :

$$\begin{aligned}
 M_g &= (\neg Q_2 \wedge \neg Q_1 \wedge \neg Q_0) \\
 M_a &= (\neg Q_2 \wedge \neg Q_1 \wedge Q_0) \\
 M_r &= (Q_2 \wedge Q_1 \wedge \neg Q_0) \vee \\
 &\quad (\neg Q_2 \wedge \neg Q_1 \wedge Q_0) \vee \\
 &\quad (Q_2 \wedge Q_1 \wedge Q_0)
 \end{aligned}$$

Notes:

Conclusions

Take away points:

- FSMs are abstract computational models, but we can use them to solve concrete problems, e.g.,
 - recognisers,
 - controllers,
 - ...
 - specifications*: like an algorithm, but more easily able to cater for asynchronous events.
- The “killer application” of FSMs for us is as a general-purpose way to realise controlled step-by-step forms of computation.
- Clearly more complex problem $\Rightarrow$ more complex solution, *but*
 - same framework and process (both conceptual, *and* practical),
 - same components (e.g., interface, implementation; data-path, control-path),
 so difference is (arguably) creativity re. design.

Notes:

Additional Reading

- ▶ *Wikipedia: Finite State Machine (FSM)*. URL: https://en.wikipedia.org/wiki/Finite-state_machine.
- ▶ D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009.
- ▶ M. Sipster. “Chapter 1: Regular languages”. In: *Introduction to the Theory of Computation*. 2nd ed. Thomson Course Technology, 2006.

Notes:

References

- [1] *Wikipedia: Finite State Machine (FSM)*. URL: https://en.wikipedia.org/wiki/Finite-state_machine (see p. 209).
- [2] D. Page. “Chapter 2: Basics of digital logic”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009 (see p. 209).
- [3] M. Sipster. “Chapter 1: Regular languages”. In: *Introduction to the Theory of Computation*. 2nd ed. Thomson Course Technology, 2006 (see p. 209).
- [4] M. Sipster. *Introduction to the Theory of Computation*. 2nd ed. Thomson Course Technology, 2006 (see pp. 5, 35–58).

Notes: